 


WEEK 4 REVIEW

Question #1


- Can we subtract numbers using only ripple carry adders?




- **No! we need additional gates**
 - Two's complement is $\text{NOT}(Y) + 1$
 - C_{in} gives us +1, but we still need to compute $\text{NOT}(Y)$

 Question #2

- Is this circuit **stable** or does it **oscillate**?




- It **oscillates!**

 

 Question #3


- Is this circuit **stable** or does it **oscillate**?



Q_T	A_T	A_{T+1}	Q_{T+1}
0	1	1	0
1	0	0	1

 Question #3

- Is this circuit **stable** or does it **oscillate**?



- It is

stable!


- $Q=0$ remains 0

Q_x	A_x
0	1
1	0

A_x	Q_{x+1}
1	0
0	1



- $Q=1$ remains 1

Rearrange the circuit...

 

Latches

  
- We overcome oscillations by combining multiple NAND or NOR gates.



- These circuits are called **latches**.

 Question #4

- Complete the truth table
 - Don't-care inputs **allowed**.
- And name the 4 possible S,R input combinations




S	R	Q_T	\bar{Q}_T	Q_{T+1}	\bar{Q}_{T+1}

← Hold
← Reset
← Set
← Forbidden

 Question #4

- Complete the truth table
 - Don't-care inputs **allowed**.
- And name the 4 possible S,R input combinations



S	R	Q_T	\bar{Q}_T	Q_{T+1}	\bar{Q}_{T+1}
0	0	0	1	0	1
0	0	1	0	1	0
0	1	X	X	0	1
1	0	X	X	1	0
1	1	X	X	0	0


← Hold
 ← Reset
 ← Set
 ← Forbidden

Summary: S'R' and SR Latches

$\bar{S}\bar{R}$ -latch

\bar{S}	\bar{R}	Q_T	\bar{Q}_T	Q_{T+1}	\bar{Q}_{T+1}
0	0	X	X	1	1
0	1	X	X	1	0
1	0	X	X	0	1
1	1	0	1	0	1
1	1	1	0	1	0

 Forbidden state
 Set Q to 1
 Reset Q to 0
 Maintain Q




"set" and "reset" cannot be both true!

SR-latch


S	R	Q_T	\bar{Q}_T	Q_{T+1}	\bar{Q}_{T+1}
0	0	0	1	0	1
0	0	1	0	1	0
0	1	X	X	0	1
1	0	X	X	1	0
1	1	X	X	0	0

 Maintain Q
 Reset Q to 0
 Set Q to 1
 Forbidden state



 
Question #5

- Given the \bar{s} input waveforms, sketch the output Q of an SR latch. Assume Q was zero initially.



Clocks

 - A periodic signal that gives timing for our circuit




- Frequency** = the number of pulses occur per second.




Clocked/Gated Latches

 - Add a new input C that acts like a "gate" over the inputs:
- If C=0 the latch ignores input
 - Maintains state.
- If C=1 the latch is "active"
 - Responds to input



 Question #6

- What are the output values from \bar{Q} and Q given the inputs on S, R and C?




S	R	C	Q	\bar{Q}
0	0	1	?	?
1	0	1		
1	0	0		
0	0	0		
0	1	0		
0	1	1		

Time →

 Question #6


- What are the output values from \bar{Q} and Q given the following inputs on S, R and C?




S	R	C	Q	\bar{Q}
			?	?
0	0	1	?	?
1	0	1	1	0
1	0	0	1	0
0	0	0	1	0
0	1	0	1	0
0	1	1	0	1

Time


Clocked SR latch behaviour

 

C	S	R	Q_{t+1}	Result
0	X	X	Q_t	hold
1	0	0	Q_t	hold
1	0	1	0	Reset
1	1	0	1	Set
1	1	1	?	undefined

 


D latch

 


- This design is good!
 - Easy to store a bit: just set D to what you want to store.
 - Can maintain state as long as C is low
 - No weird forbidden inputs.

D latch is transparent

 - Any changes to its inputs are visible to the output when control signal (Clock) is 1.
 - Output keeps toggling back and forth.




 - We want output to change exactly once per cycle.




Flip-flops

 - Positive edge:
triggered on rising edge of the clock





 - Negative edge:
triggered on falling edge of the clock



  
Question #6

- Assuming all inputs start low, complete the timing diagram



Flip-flops

 - For input to propagate to output, it takes each of the latches to be active once.
- First latch changes on “**flip**”.
- Output can only change upon “**flip**”, which is basically the falling edge of the clock signal
- At most one change per clock cycle




Flip-flops

- We have:
 - D flip-flops (most common type!)
 - SR flip-flops
 - T flip-flops (for “toggle”)
 - JK flip-flops

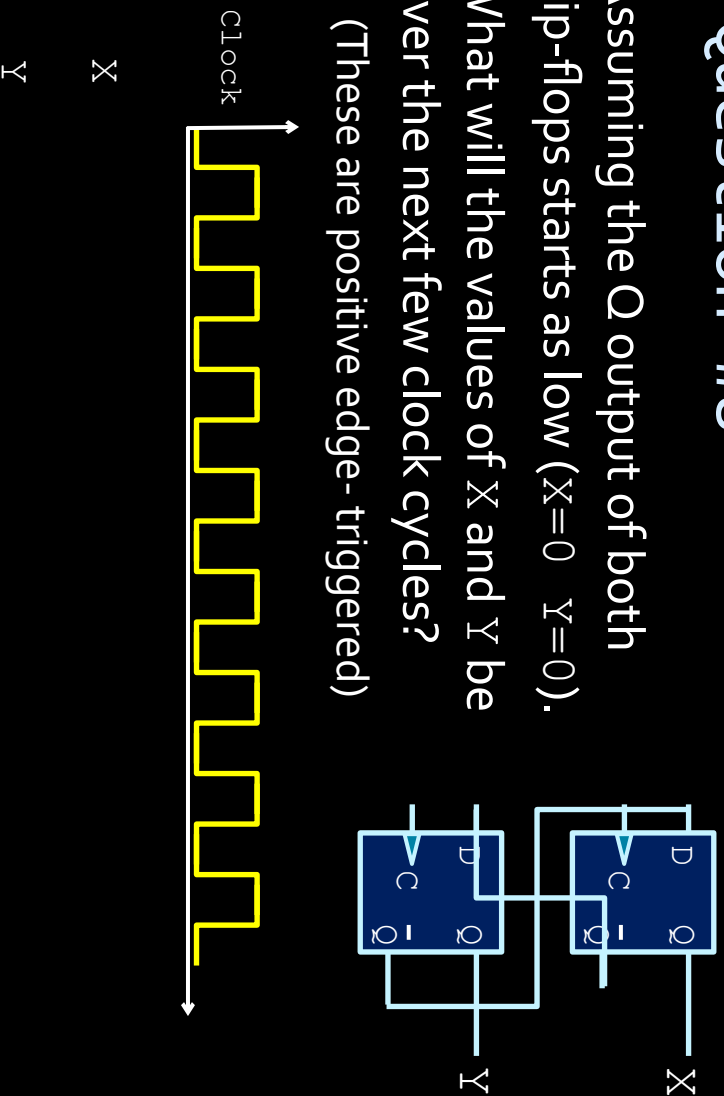
Question #8

- Assuming the Q output of both flip-flops starts as low ($X=0$ $Y=0$).
- What will the values of X and Y be over the next few clock cycles?
 - (These are positive edge-triggered)



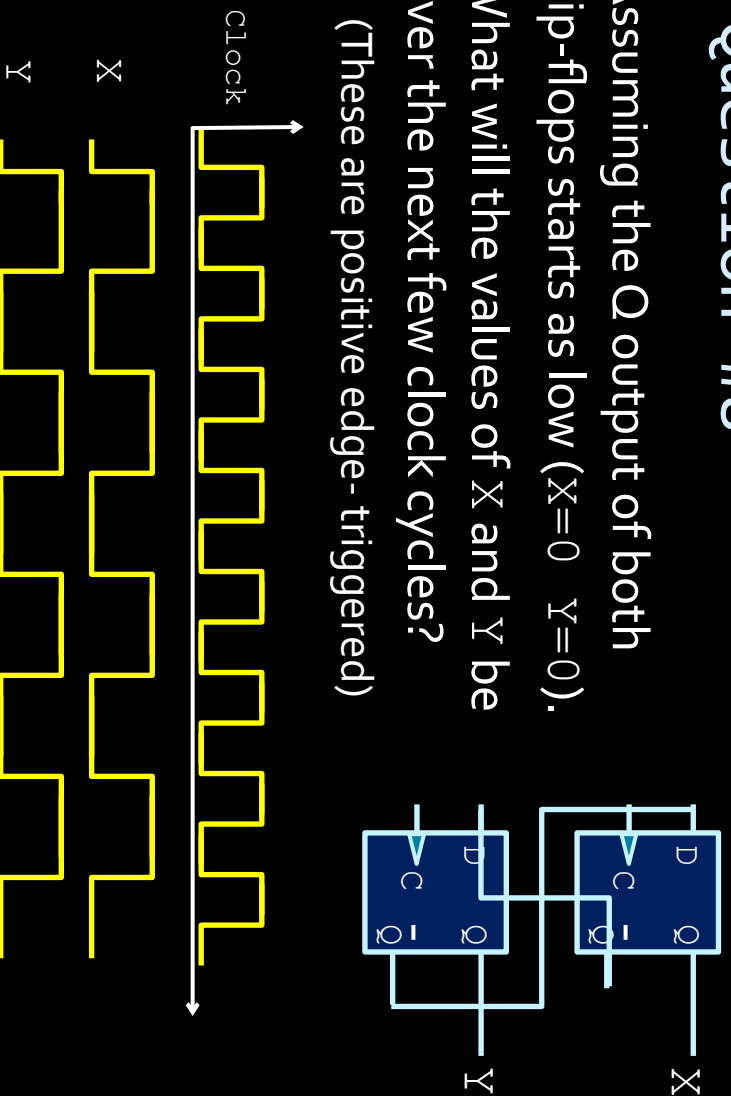
Question #8

- Assuming the Q output of both flip-flops starts as low ($X=0$ $Y=0$).
- What will the values of X and Y be over the next few clock cycles?
 - (These are positive edge-triggered)



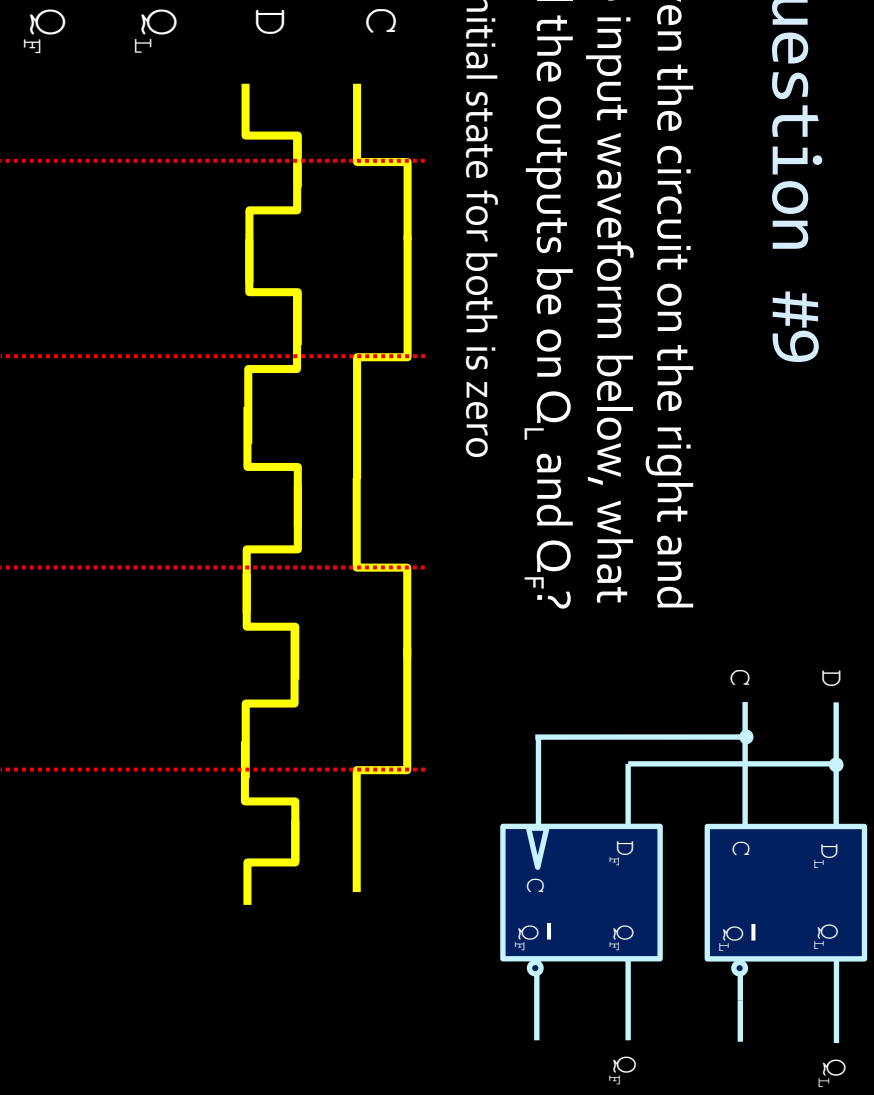Question #9

- Given the circuit on the right and the input waveform below, what will the outputs be on Q_L and Q_F ?
- Initial state for both is zero



Question #9

- Given the circuit on the right and the input waveform below, what will the outputs be on Q_L and Q_F ?
- Initial state for both is zero

