

# Week 3 Part E: Comparators

$$F = A \cdot H + \bar{A} \cdot C$$

Corporate needs you to find the differences between this picture and this picture.

They're the same picture.



# Comparators

- A circuit that takes in two input vectors, and determines if the first is greater than, less than or equal to the second.
- How does one make such a circuit?



# Basic Comparators

- Consider two one-bit binary numbers A and B.
- The circuits for this would be:

□  $A=B$ :


$$A \cdot B + \bar{A} \cdot \bar{B}$$

□  $A>B$ :

$$A \cdot \bar{B}$$

□  $A<B$ :

$$\bar{A} \cdot B$$

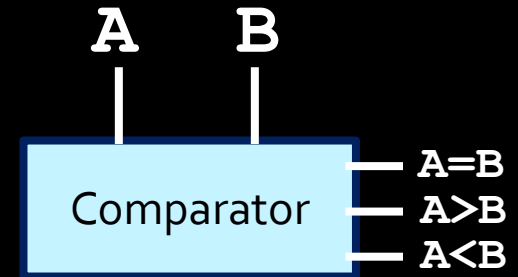


A	B	
0	0	==
0	1	<
1	0	>
1	1	==


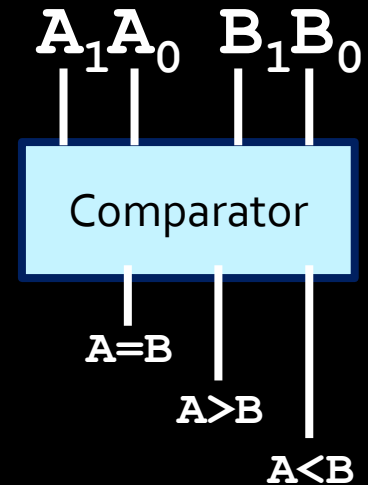
# Basic Comparators

- What if A and B are two bits long?
- The terms for this circuit for have to expand to reflect the additional bit.
- For example:




□  $A==B$ :

$$(A_1 \cdot B_1 + \bar{A}_1 \cdot \bar{B}_1) \cdot (A_0 \cdot B_0 + \bar{A}_0 \cdot \bar{B}_0)$$

Make sure that the values  
of bit 1 are the same




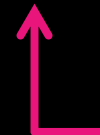Make sure that the values  
of bit 0 are the same


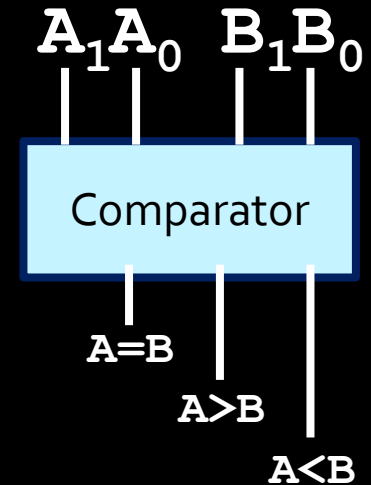
# Basic Comparators

- What about checking if A is greater or less than B?



□  $A>B$ :

$$A_1 \cdot \bar{B}_1 + (A_1 \cdot B_1 + \bar{A}_1 \cdot \bar{B}_1) \cdot (A_0 \cdot \bar{B}_0)$$

Check if first bit satisfies condition

If not, check that the first bits are equal...


...and then do the 1-bit comparison

□  $A<B$ :

$$\bar{A}_1 \cdot B_1 + (A_1 \cdot B_1 + \bar{A}_1 \cdot \bar{B}_1) \cdot (\bar{A}_0 \cdot B_0)$$



# Basic Comparators

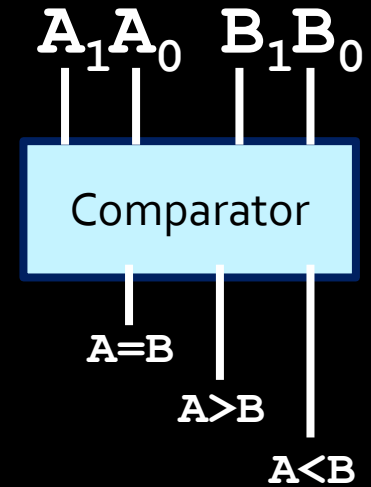

- The final circuit equations for two-input comparators are shown below.
  - Note the sections they have in common!

□  $A==B$ :

$$(A_1 \cdot B_1 + \bar{A}_1 \cdot \bar{B}_1) \cdot (A_0 \cdot B_0 + \bar{A}_0 \cdot \bar{B}_0)$$

□  $A>B$ :

$$A_1 \cdot \bar{B}_1 + (A_1 \cdot B_1 + \bar{A}_1 \cdot \bar{B}_1) \cdot (A_0 \cdot \bar{B}_0)$$

□  $A<B$ :

$$\bar{A}_1 \cdot B_1 + (A_1 \cdot B_1 + \bar{A}_1 \cdot \bar{B}_1) \cdot (\bar{A}_0 \cdot B_0)$$



# General Comparators

- The general circuit for comparators requires you to define equations for each case.
- Case #1: Equality
  - If inputs A and B are equal, then all bits must be the same.
  - Define  $X_i$  for any digit  $i$ :
    - (equality for digit  $i$ )
  - Equality between A and B is defined as:

$$X_i = A_i \cdot B_i + \bar{A}_i \cdot \bar{B}_i$$

$$A==B : X_0 \cdot X_1 \cdot \dots \cdot X_n$$



# What about $A > B$ , $A < B$ ?

- Suppose we have two 6-bit numbers.
- Suppose  $A_5=B_5$  and  $A_4=B_4$ 
  - This means  $X_5=1$ ,  $X_4=1$
- If  $A_3=1$  and  $B_3=0$  then  $A > B$ 
  - Regardless of digits 2,1,0.
- If  $A_3=0$  and  $B_3=1$  then  $A < B$ 
  - Regardless of digits 2,1,0.
- If  $A_3=B_3$  then we need to check digit 2...
  - Note  $A_3=B_3$  means  $X_3=1$





# Generalize!

- Case #2:  $A > B$

- The first non-matching bits occur at bit  $i$ , where  $A_i=1$  and  $B_i=0$ . All higher bits match.
- Using the definition for  $X_i$  from before:

$$A > B = A_n \cdot \bar{B}_n + X_n \cdot A_{n-1} \cdot \bar{B}_{n-1} + \dots + A_0 \cdot \bar{B}_0 \cdot \prod_{k=1}^n X_k$$

- Case #3:  $A < B$

- The first non-matching bits occur at bit  $i$ , where  $A_i=0$  and  $B_i=1$ . Again, all higher bits match.

$$A < B = \bar{A}_n \cdot B_n + X_n \cdot \bar{A}_{n-1} \cdot B_{n-1} + \dots + \bar{A}_0 \cdot B_0 \cdot \prod_{k=1}^n X_k$$



# Example for 4 bits

$A=B$

$$A=B = X_3 \cdot X_2 \cdot X_1 \cdot X_0$$

$$X_i = A_i \cdot B_i + \bar{A}_i \cdot \bar{B}_i$$

$A > B$

$$A_3 \cdot \bar{B}_3 + X_3 \cdot A_2 \cdot \bar{B}_2 + X_3 \cdot X_2 \cdot A_1 \cdot \bar{B}_1 + X_3 \cdot X_2 \cdot X_1 \cdot A_0 \cdot \bar{B}_0$$

$A < B$

$$\bar{A}_3 \cdot B_3 + X_3 \cdot \bar{A}_2 \cdot B_2 + X_3 \cdot X_2 \cdot \bar{A}_1 \cdot B_1 + X_3 \cdot X_2 \cdot X_1 \cdot \bar{A}_0 \cdot B_0$$



# Comparator truth table

- Given two input vectors of size  $n=2$ , output of circuit is shown at right.

Inputs				Outputs		
$A_1$	$A_0$	$B_1$	$B_0$	$A < B$	$A = B$	$A > B$
0	0	0	0	0	1	0
0	0	0	1	1	0	0
0	0	1	0	1	0	0
0	0	1	1	1	0	0
0	1	0	0	0	0	1
0	1	0	1	0	1	0
0	1	1	0	1	0	0
0	1	1	1	1	0	0
1	0	0	0	0	0	1
1	0	0	1	0	0	1
1	0	1	0	0	1	0
1	0	1	1	1	0	0
1	1	0	0	0	0	1
1	1	0	1	0	0	1
1	1	1	0	0	0	1
1	1	1	1	0	1	0



# Comparator example (cont'd)

$A < B$ :

	$\overline{B}_0 \cdot \overline{B}_1$	$B_0 \cdot \overline{B}_1$	$B_0 \cdot B_1$	$\overline{B}_0 \cdot B_1$
$\overline{A}_0 \cdot \overline{A}_1$	0	1	1	1
$A_0 \cdot \overline{A}_1$	0	0	1	1
$A_0 \cdot A_1$	0	0	0	0
$\overline{A}_0 \cdot A_1$	0	0	1	0

$$LT = B_1 \cdot \overline{A}_1 + B_0 \cdot B_1 \cdot \overline{A}_0 + B_0 \cdot \overline{A}_0 \cdot \overline{A}_1$$



# Comparator example (cont'd)

$A=B :$

	$\overline{B}_0 \cdot \overline{B}_1$	$B_0 \cdot \overline{B}_1$	$B_0 \cdot B_1$	$\overline{B}_0 \cdot B_1$
$\overline{A}_0 \cdot \overline{A}_1$	1	0	0	0
$A_0 \cdot \overline{A}_1$	0	1	0	0
$A_0 \cdot A_1$	0	0	1	0
$\overline{A}_0 \cdot A_1$	0	0	0	1

$$EQ = \overline{B}_0 \cdot \overline{B}_1 \cdot \overline{A}_0 \cdot \overline{A}_1 + B_0 \cdot \overline{B}_1 \cdot A_0 \cdot \overline{A}_1 + \\ B_0 \cdot B_1 \cdot A_0 \cdot A_1 + \overline{B}_0 \cdot B_1 \cdot \overline{A}_0 \cdot A_1$$



# Comparator example (cont'd)

$A > B$  :


	$\overline{B}_0 \cdot \overline{B}_1$	$B_0 \cdot \overline{B}_1$	$B_0 \cdot B_1$	$\overline{B}_0 \cdot B_1$
$\overline{A}_0 \cdot \overline{A}_1$	0	0	0	0
$A_0 \cdot \overline{A}_1$	1	0	0	0
$A_0 \cdot A_1$	1	1	0	1
$\overline{A}_0 \cdot A_1$	1	1	0	0

$$GT = \overline{B}_1 \cdot A_1 + \overline{B}_0 \cdot \overline{B}_1 \cdot A_1 + \overline{B}_0 \cdot A_0 \cdot A_1$$


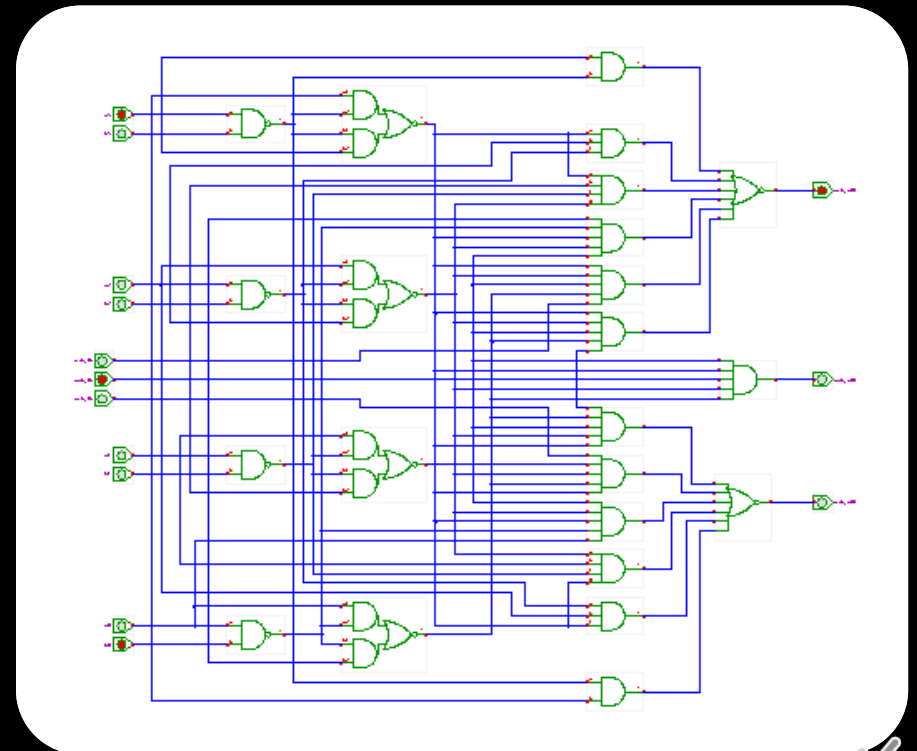
# Comparing larger numbers

- As numbers get larger, the comparator circuit gets more complex.
- For large numbers, it can be easier to simply subtract and check the sign of the result.
  - Easier, less circuitry, just not faster.



# A Summary

- We learned several combinatorial devices:
  - Control the flow of a signal: Mux, demux
  - Translate signals, control output: decoder
  - Arithmetic: adder, subtractor, comparator.
- Next week we'll work with sequential circuits: circuits that have memory.

