

# Logic Gates and Circuits

## CSCB58: Computer Organization

Lecture 1: January 7th, 2025



Computer Science  
UNIVERSITY OF TORONTO

# A little bit about your instructor

**Nandita Vijaykumar**

- Assistant Professor in the Computer Science Department at UofT and UTSC, since 2020
- PhD from Carnegie Mellon University
- Worked at Intel, AMD, Microsoft, and Nvidia
- Best way to reach me: [nandita@cs.toronto.edu](mailto:nandita@cs.toronto.edu)
- My research group: embARC Lab ([www.embarclab.com](http://www.embarclab.com))
- Our research: computer systems + architecture
  - Cross-layer spanning applications, systems, and hardware
  - Application-specific: E.g., machine learning, graphics, HPC, robotics




# My research group: embARC



# Today!

- **Why take B58?**
- **What's in B58?**
- **How does the course work?**
- **Logic gates and circuits**

# The course at a glance...

 

# CSCB58 Is Intense

- **There is a lot to learn, practice, and do.**
- **You have tasks every week.**
- **It is historically one of the busiest courses for students.**
- **But there is good news:**
  - **Material not hard to understand, but it does require practice and effort.**
  - **All this practice makes you really good.**
  - **Course grade tend to skew high**



# What is a computer?



do you need  
electricity for a  
computer?

# CSCB58 Asks the Big Questions

- What is a computer?
- What is memory? How does a computer store information
- Why do computers work in binary?
- how does a computer actually... compute?
- How does the code we write in Python/Java/C++/etc actually translate into things happening?



# Why take CSCB58?

- To better understand computers!
- See what's going on "under the hood"
- Open the black box, get rid of the mystery
- Understand the whole pipeline, from atoms to assembly
  - Everything above assembly is virtualization and abstraction
  - Everything else is an **illusion!**
- Build a cool software-based project!

# CSCB58 Course Goals

- Learn to **build computers...**
  - Understand and design the underlying architecture of computer systems.
- ... and **how they work.**
  - How programs use digital structures to do computation.
- Learn **engineering.**
  - Build systems from components, understand abstractions, make tradeoffs.
- Learn **there is no magic!**
  - There is nothing you cannot understand.


# CSCB58 Course Goals

- By the end of this course, you will be able to build a computer from the atomic level upwards\*
  - Build circuits from logic gates
  - Build memory/computational units from circuits
  - Build a computer from memory/computational units

(\* Given an infinite amount of time, and the ability to manipulate individual atoms.)
 
# Build a Computer!

- ...from LEGO
- ...in Minecraft
- ...from living crabs\*
  - \* Do not build a computer from live crabs. It is unethical.
- ...inside an iMessage to break into iPhones\*\*
  - \*\* also unethical.



# Some Admin



<https://villains.fandom.com/wiki/Vogons>

# Administrivia

- **This course is on Quercus: [q.utoronto.ca](http://q.utoronto.ca)**
  - Check it regularly!
- **Get help on Piazza**
  - Use for all assignment or technical questions.
  - Read pinned posts (first posts at the top) before asking questions!
  - Private posts for questions relating to you only
- **E-mail (use official email only!)**
  - **Only for emergencies and confidential personal matters**
- **Office hours**
  - Dedicated lab office hours by TAs (for lecture material, labs, and assignments)
  - Instructor office hours (for lecture material and personal situations)



# Course Components

- **Lectures**
  - 2 hour in person lectures every week on Tuesday
  - No TUT sessions
- **Quizzes** **10%**
  - 11 short weekly quizzes on Mondays (starting next week)
- **Labs** **40%**
  - 5 labs starting this week (first is very easy, don't worry)
- **Project** **17%**
  - 3-week assembly project
- **Final exam** **33%**
  - Final exam - **must get 30% to pass the course**

# Administrivia

- **Some general principles for how we will operate:**
- **No exceptions other than AccessAbility and for medical emergencies**
- **We want consistent and fair policies for all!**
- **Course requirements: All requirements and prerequisites must be met**

# Labs Marking

- **Submit each lab solution to Quercus at each due date (TBD)**
  - **Usually a Logisim file, sometimes also a PDF.**
  - **Late? You will lose marks.**
- **Each student has bi-weekly 10-minute interview slot with your TA to demonstrate:**
  - **... your solution.**
  - **... basic understanding of the material.**  
**(by answering oral questions from the TA).**
  - **Your mark is based on both!**

# Missed Term Work

- Life happens. We understand.
- We give you justification-free tokens.
- Can miss/do badly on 2 quizzes and 1 lab.
  - For any reason. We don't need to know.
- Works automatically, no need to tell us.
  - We drop lowest 2 quizzes and lowest 1 lab
  - You just focus on getting better.
- Do not waste or abuse them!
  - **We will not give extra "tokens", no matter what.**
  - Best strategy: show up and do your best.
- No make up for late work. Late = missed.

# How to Succeed in Labs?

- **The labs are not hard, but they require work.**
- **Labs are your chance to practice.**  
**Do the work yourself.**
  - **Submit something meaningful and on time.**
- **Don't plagiarize**
  - **You won't be able to answer TA questions...**
  - **... or answer the next quiz ...**
  - **... or the final exam.**

# Lab Software

- Lab 1-3 use Logisim-evolution for hardware.
  - Lab 1 will tell you all you need to know.
  - Do not use the original Logisim or its other variations of it. Use the in the lab PDF file or the link above.
- Labs 4-5 will use MARS simulator for MIPS assembly.
  - Same idea: link will be included.



# Project

- **Multi-week assembly programming project.**
- **Worth 17%**
- **At the end of the course.**
- **Done individually.**
- **Marking based on:**
  - **Short project report and video.**
  - **Submitted code**
- **Details will follow later.**


# Final Exam

- **Worth 33%**
- **Closed book.**
- **In-person**
- **Details will follow.**


# How to do well in CSCB58

- **Be Interested!**
- **Put in the effort:**
  - **Do labs!**
  - **Practice solving lecture questions on your own.**
  - **Study.**
  - **“In theory there’s no difference between practice and theory, but in practice there usually is”**
- **Interact**
  - **lectures, labs (TAs), Piazza**
  - **Ask questions in Piazza or review sessions.**

# This week

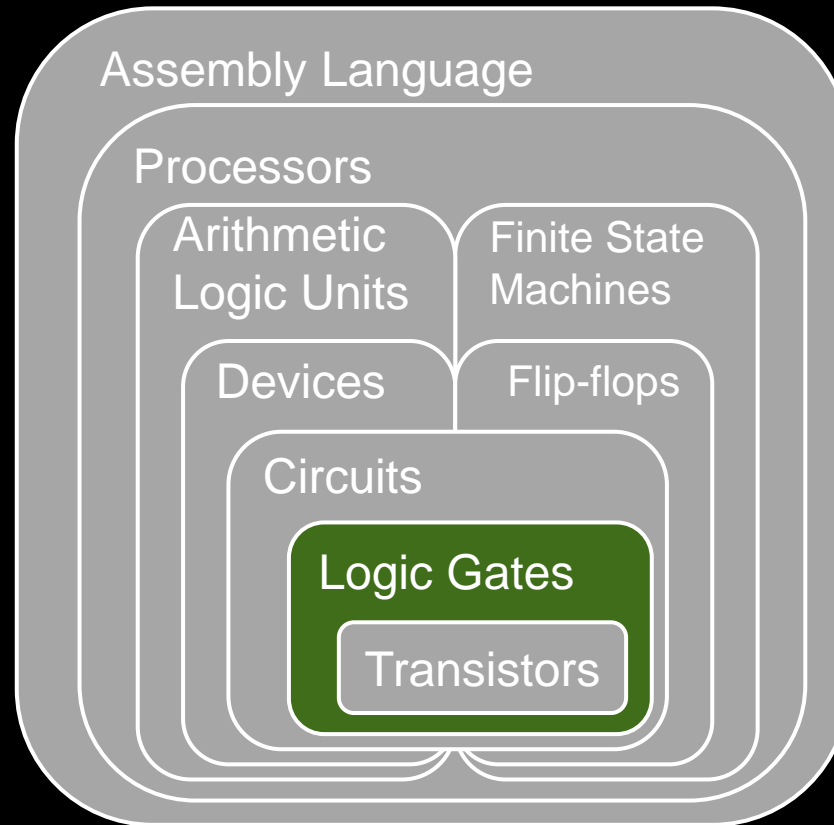

 You already know some important concepts...




# Boolean Logic from CSCA67

- Example: Create an expression that is true if both variables A and B are true, or if both C and D are true.

$$G = A \ \& \ B \ | \ C \ \& \ D$$

 
- Now create a circuit that does the same thing:





 
# Logic Gates

- If you know how to create simple logical expressions, you already know the basics of putting logic gates together to form simple circuits.
- Just need to know which logic operations are represented by which gate!



# AND Gate

 


**truth table**  
For every combination of **inputs**, what are the **outputs**?

inputs		outputs
A	B	Y
0	0	0
0	1	0
1	0	0
1	1	1


If the truth table for two circuits is the same, they are equivalent

# OR Gate

 


A	B	Y
0	0	0
0	1	1
1	0	1
1	1	1

# NOT Gates

 


A	Y
0	1
1	0

# XOR Gates

 

A	B	Y
0	0	0
0	1	1
1	0	1
1	1	0


# NAND Gates

 

A	B	Y
0	0	1
0	1	1
1	0	1
1	1	0




# NOR Gates

 

A	B	Y
0	0	1
0	1	0
1	0	0
1	1	0

# Buffer

 


This is not as silly as you might think now, as we'll see later...

A	Y
0	0
1	1
 
# Circuit Design?

- Creating circuit logic can be similar to creating Boolean logic in Python, C or Java:

```
Y = (!A and !B and !C) or  
    (!A and B and C) or  
    (A and B and C)
```




# The real challenge in circuit design...

- Given a truth table or description...
- ...find a circuit that implements it.
- Many ways of tackling the problem

A	B	C	Y
0	0	0	1
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	1

# You are here

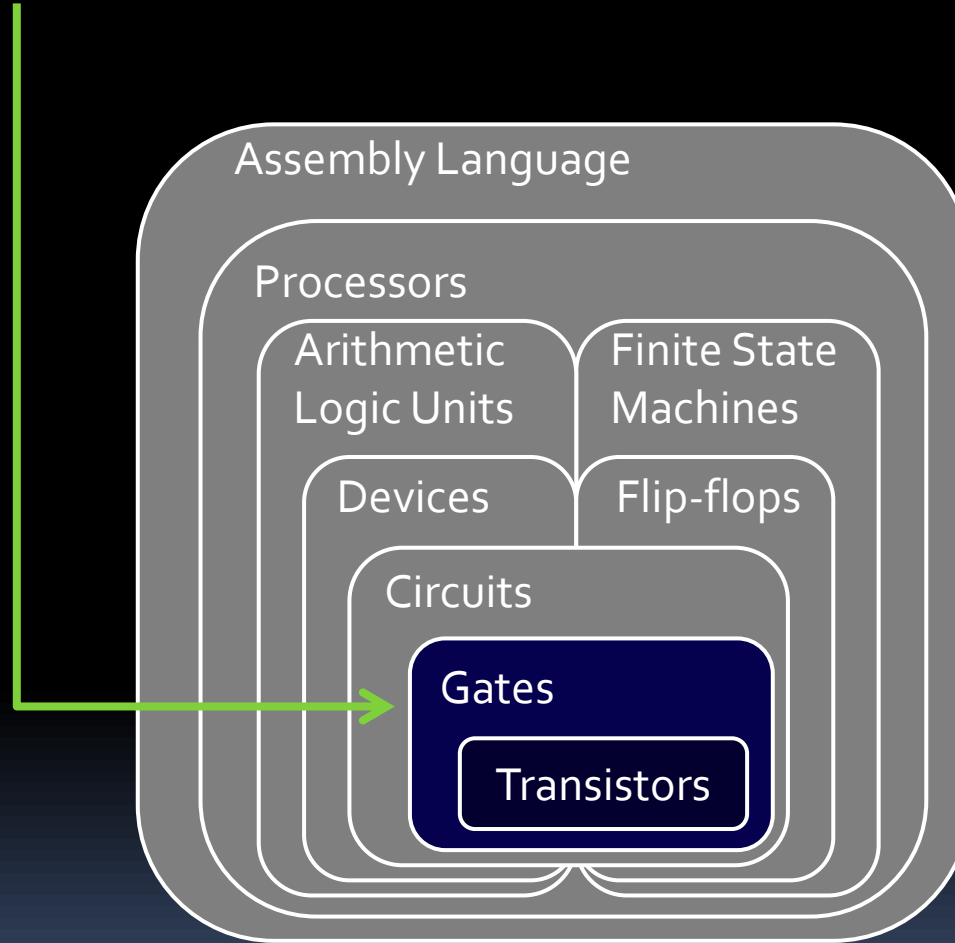

# Making logic with gates

- Logic gates create an output value, based on one or more input values.
- These correspond to Boolean logic that we've seen before in CSCAo8/A48/A67:

AND



A	B	Y
0	0	0
0	1	0
1	0	0
1	1	1

OR



A	B	Y
0	0	0
0	1	1
1	0	1
1	1	1

NOT



A	Y
0	1
1	0


# Other gates

XOR



A	B	Y
0	0	0
0	1	1
1	0	1
1	1	0

NAND

 

A	B	Y
0	0	1
0	1	1
1	0	1
1	1	0

NOR



A	B	Y
0	0	1
0	1	0
1	0	0
1	1	0

# Aside: notation

- While we're talking about notation...
  - **AND** operations are denoted in these expressions by the multiplication symbol.
    - e.g.  $A \cdot B \cdot C$  or  $ABC$  or  $A * B * C \approx A \wedge B \wedge C$
  - **OR** operations are denoted by the addition symbol.
    - e.g.  $A + B + C \approx A \vee B \vee C$
  - **NOT** is denoted by multiple symbols.
    - e.g.  $!A$  or  $\sim A$  or  $\bar{A}$  or  $A'$  or  $\neg A$
  - **XOR** occurs rarely in circuit expressions.
    - e.g.  $A \oplus B$




# Making Boolean expressions


- So how would you represent boolean expressions using logic gates?

$$Y = (A \text{ or } B) \text{ and } (\text{not } A \text{ or not } B) \text{ or } C$$

- Like so:

 


# Now you are here

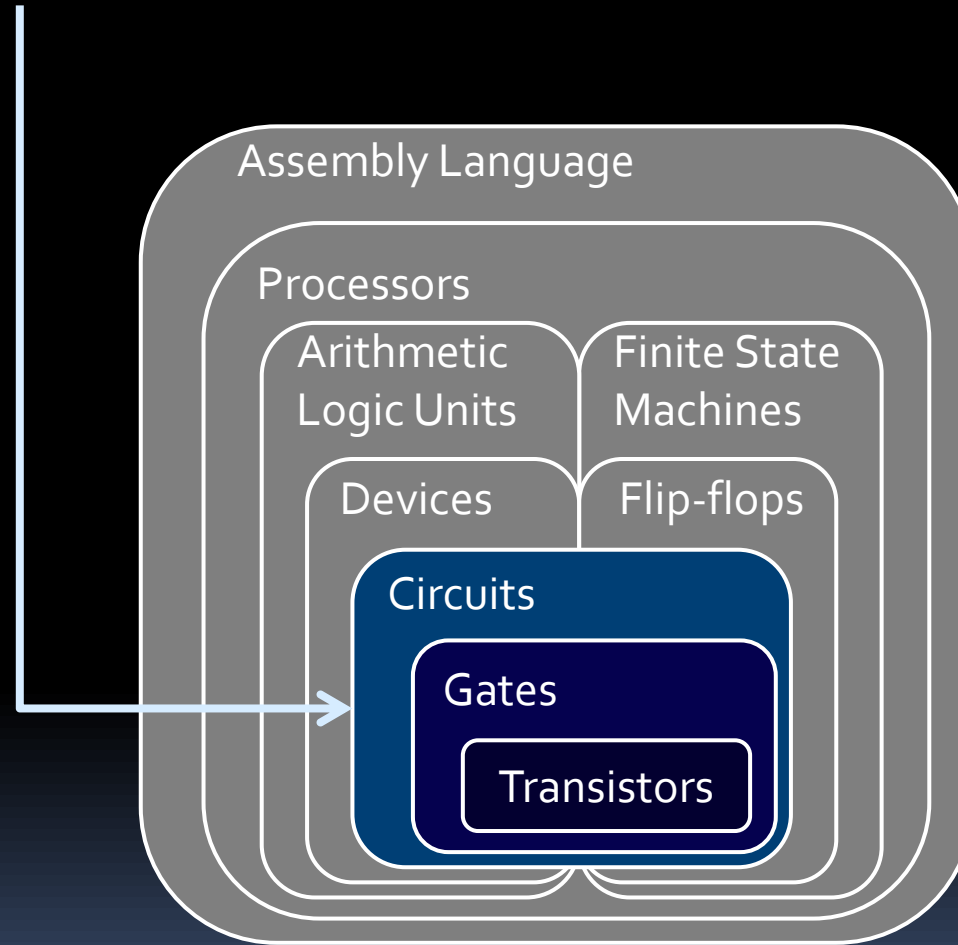

 
# Creating complex circuits

- What do we do in the case of more complex circuits, with several inputs and more than one output?
  - If you're lucky, a truth table is provided to express the circuit.
  - Usually the behaviour of the circuit is expressed in words, and the first step involves creating a truth table that represents the described behaviour.


 
# Circuit example

- The circuit on the right has three inputs (A, B and C) and two outputs (X and Y).



- What logic is needed to set X high when all three inputs are high?
- What logic is needed to set Y high when the number of high inputs is odd?

# Combinational circuits


- Small problems can be solved easily.



- Larger problems require a more systematic approach.
  - ▣ Example: Given three inputs A, B, and C, make output Y high in the case where all of the inputs are low, or when A and B are low and C is high, or when A and C are low but B is high, or when A is low and B and C are high.
 
# Creating complex logic

- How do we approach problems like these (and circuit problems in general)?
- **Basic steps:**
  1. Create truth tables.
  2. Express as Boolean expression.
  3. Convert to gates.
- The key to an efficient design?
  - Spending extra time on Step #2.



# Example truth table

- Consider the following example:
  - *"Given three inputs  $A$ ,  $B$ , and  $C$ , make output  $Y$  high wherever any of the inputs are low, except when all three are low or when  $A$  and  $C$  are high."*
  - This leads to the truth table on the right.
  - Is there a **more compact way** to describe this function?

A	B	C	Y
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	1
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	0

# Warm-Up Exercise

For each of the following logic expressions, what are the A, B, C values that make the expression evaluate to 1 ?

$A'B'C'$

$ABC$

$A'BC$

$ABC'$



# Answers to Warm-Up Exercise

For each of the following logic expressions, what are the A, B, C values that make the expression evaluate to 1?

$A'B'C'$

- A=0, B=0, C=0, and only this!

$ABC$

- 111 and only this!

$A'BC$


- 011 and only this!

$ABC'$

- 110 and only this!

# Maxterms, informally


- Assume a standard truth table format.
  - Sort rows as if input ABC is binary number.
- Maxterms tell us **which rows have low output**.
  - These rows are referred to as **maxterms**.
- Express circuit behaviour by listing those rows.
  - In this example, we only need maxterms  $M_0$   $M_5$   $M_7$

Row index	A	B	C	Y		Maxterm	Y
0	0	0	0	0		$M_0$	0
1	0	0	1	1		$M_1$	1
2	0	1	0	1		$M_2$	1
3	0	1	1	1		$M_3$	1
4	1	0	0	1		$M_4$	1
5	1	0	1	0		$M_5$	0
6	1	1	0	1		$M_6$	1
7	1	1	1	0		$M_7$	0

# Minterms, informally

- A more popular alternative:  
list which input rows cause **high output**.
  - These rows are referred to as **minterms**.
  - In this case we have the minterms  $m_1$   $m_2$   $m_3$   $m_4$   $m_6$

Row index	A	B	C	Y
0	0	0	0	0
1	0	0	1	1
2	0	1	0	1
3	0	1	1	1
4	1	0	0	1
5	1	0	1	0
6	1	1	0	1
7	1	1	1	0



Minterm	Y
$m_0$	0
$m_1$	1
$m_2$	1
$m_3$	1
$m_4$	1
$m_5$	0
$m_6$	1
$m_7$	0

# Minterms and maxterms

- A more formal description:
  - **minterm** = an AND expression with every input present in true or complemented form.
  - **maxterm** = an OR expression with every input present in true or complemented form.
- For example, given four inputs (A, B, C, D):
  - Valid minterms:
    - $A \cdot B \cdot \bar{C} \cdot D$ ,  $A \cdot \bar{B} \cdot C \cdot \bar{D}$ ,  $A \cdot B \cdot C \cdot D$
  - Valid maxterms:
    - $A+B+\bar{C}+D$ ,  $A+\bar{B}+C+\bar{D}$ ,  $A+B+C+D$
  - Neither minterm nor maxterm:
    - $A \cdot B+C \cdot D$ ,  $A \cdot B \cdot D$ ,  $A+B$

# Naming

- Given  $n$  inputs, there are  $2^n$  minterms and maxterms possible (same as rows in a truth table).
  - **minterms** are labeled as  $m_x$   
**maxterms** are labeled as  $M_x$ 
    - The  $x$  subscript indicates the row in the truth table.
    - $x$  starts at 0 and ends with  $n-1$ .
  - Minterms are about when output is 1:
    - From  $m_0$  for  $\bar{A} \cdot \bar{B} \cdot \bar{C}$  to  $m_7$  for  $A \cdot B \cdot C$
  - Maxterms are about when output is 0:
    - $M_0 (A+B+C)$  to  $M_7 (\bar{A}+\bar{B}+\bar{C})$
- }  $n=3$

## $m_0$ vs $M_0$

- Minterm  $m_0$  is  $\bar{A}$  and  $\bar{B}$  and  $\bar{C}$ 
  - $m_0 = 1$  if and only if:  $A = B = C = 0$  (row 0)
- Maxterm  $M_0$  is  $A$  or  $B$  or  $C$ 
  - $M_0 = 0$  if and only if:  $A = B = C = 0$  (row 0)
- **Minterms** tell us when **the output is 1**
- **Maxterms** tell us when **the input is 0**

# Examples

For example, given four inputs (A, B, C, D):

- Valid minterms:
  - $A \cdot B \cdot \bar{C} \cdot D$   $m_{13}$  (because  $1101 = 13$ )
  - $A \cdot \bar{B} \cdot C \cdot \bar{D}$   $m_{10}$  (because  $1010 = 10$ )
  - $A \cdot B \cdot C \cdot D$   $m_{15}$  (because  $1111 = 15$ )
- Valid maxterms:
  - $A+B+\bar{C}+D$   $M_2$  (because  $0010 = 2$ )
  - $A+\bar{B}+C+\bar{D}$   $M_5$  (because  $0101 = 5$ )
  - $A+B+C+D$   $M_0$  (because  $0000 = 0$ )
- Neither minterm nor maxterm:
  - $A \cdot B+C \cdot D$  mixes AND and OR
  - $A \cdot B \cdot D$
  - $A+B$  missing some of the inputs

# Quick Exercises

- Given 4 inputs  $\underline{A}, \underline{B}, C$  and  $D$  write:

- $m_9 \Rightarrow$

- $m_{15} \Rightarrow$

- $m_{16} \Rightarrow$

- $M_2 \Rightarrow$

- Which minterm is this?

- $\overline{A} \cdot B \cdot \overline{C} \cdot \overline{D}$

- Which maxterm is this?

- $A+B+C+\overline{D}$



# What is This For?

- Recap:
  - Minterms and maxterms are a shorthand to refer to **rows of the truth table**.
  - **minterms** describe rows where output is **high**.
  - **maxterms** describe rows where output is **low**.
- Use minterms and maxterms to go from truth table to logic expression
  - Define output by **OR-ing minterms** or **AND-ing maxterms**.
  - Don't mix them both

# Using minterms and maxterms

- What are minterms used for?
  - A single minterm indicates a set of inputs that will make the output go high.
  - Example:  $m_2$
  - Output **only goes high in third row** of truth table.

Row index	A	B	C	D	$m_2$
0	0	0	0	0	0
1	0	0	0	1	0
2	0	0	1	0	1
3	0	0	1	1	0
4	0	1	0	0	0
5	0	1	0	1	0
6	0	1	1	0	0
7	0	1	1	1	0
8	1	0	0	0	0
9	1	0	0	1	0
10	1	0	1	0	0
11	1	0	1	1	0
12	1	1	0	0	0
13	1	1	0	1	0
14	1	1	1	0	0
15	1	1	1	1	0

# Using minterms and maxterms

- What happens when you **OR** two **minterms**?
- Result is output that goes high in both minterm cases.
- **For  $m_2+m_8$ , both third and ninth rows** of truth table result in high output.

	A	B	C	D	$m_2$	$m_8$	$m_2+m_8$
0	0	0	0	0	0	0	
1	0	0	0	1	0	0	
2	0	0	1	0	1	0	
3	0	0	1	1	0	0	
4	0	1	0	0	0	0	
5	0	1	0	1	0	0	
6	0	1	1	0	0	0	
7	0	1	1	1	0	0	
8	1	0	0	0	0	1	
9	1	0	0	1	0	0	
10	1	0	1	0	0	0	
11	1	0	1	1	0	0	
12	1	1	0	0	0	0	
13	1	1	0	1	0	0	
14	1	1	1	0	0	0	
15	1	1	1	1	0	0	

# Creating Boolean expressions

- Two canonical forms of Boolean expressions:
- **Sum-of-Minterms** (SOM):
  - Since each minterm corresponds to a single high output in the truth table, the combined high outputs are a **union** of these minterm expressions.
  - Also known as: Sum-of-Products.
- **Product-of-Maxterms** (POM):
  - Since each maxterm only produces a single low output in the truth table, the combined low outputs are an **intersection** of these maxterm expressions.
  - Also known as Product-of-Sums.

$$Y = m_2 + m_6 + m_7 + m_{10} \quad (\text{SOM})$$

	A	B	C	D	$m_2$	$m_6$	$m_7$	$m_{10}$	Y
0	0	0	0	0					
1	0	0	0	1					
2	0	0	1	0					
3	0	0	1	1					
4	0	1	0	0					
5	0	1	0	1					
6	0	1	1	0					
7	0	1	1	1					
8	1	0	0	0					
9	1	0	0	1					
10	1	0	1	0					
11	1	0	1	1					
12	1	1	0	0					
13	1	1	0	1					
14	1	1	1	0					
15	1	1	1	1					

$$Y = m_2 + m_6 + m_7 + m_{10} \quad (\text{SOM})$$

	A	B	C	D	$m_2$	$m_6$	$m_7$	$m_{10}$	Y
0	0	0	0	0	0	0	0	0	0
1	0	0	0	1	0	0	0	0	0
2	0	0	1	0	1	0	0	0	1
3	0	0	1	1	0	0	0	0	0
4	0	1	0	0	0	0	0	0	0
5	0	1	0	1	0	0	0	0	0
6	0	1	1	0	0	1	0	0	1
7	0	1	1	1	0	0	1	0	1
8	1	0	0	0	0	0	0	0	0
9	1	0	0	1	0	0	0	0	0
10	1	0	1	0	0	0	0	1	1
11	1	0	1	1	0	0	0	0	0
12	1	1	0	0	0	0	0	0	0
13	1	1	0	1	0	0	0	0	0
14	1	1	1	0	0	0	0	0	0
15	1	1	1	1	0	0	0	0	0

$$Y = M_3 \cdot M_5 \cdot M_7 \cdot M_{10} \cdot M_{14} \quad (\text{POM})$$

A	B	C	D	M <sub>3</sub>	M <sub>5</sub>	M <sub>7</sub>	M <sub>10</sub>	M <sub>14</sub>	Y
0	0	0	0						
0	0	0	1						
0	0	1	0						
0	0	1	1						
0	1	0	0						
0	1	0	1						
0	1	1	0						
0	1	1	1						
1	0	0	0						
1	0	0	1						
1	0	1	0						
1	0	1	1						
1	1	0	0						
1	1	0	1						
1	1	1	0						
1	1	1	1						

$$Y = M_3 \cdot M_5 \cdot M_7 \cdot M_{10} \cdot M_{14} \quad (\text{POM})$$

[illegible]



# Using Sum-of-Minterms

- Sum-of-Minterms is a way of expressing which inputs cause the output to go high. Product-of-Maxterms is a way of expression which inputs cause the output to go low.
  - Assumes that the truth table columns list the inputs according to some logical or natural order.
- Minterm and maxterm expressions are used for efficiency reasons:
  - More compact than displaying entire truth tables.
  - Sum-of-minterms (SOM) are useful when very few input combinations that produce high output.
  - Product-of-maxterms (POM) useful when expressing truth tables that have very few low output cases.

# Converting SOM to gates

- Once you have a Sum-of-Minterms expression, it is easy to convert this to the equivalent combination of gates:

$$m_0 + m_1 + m_2 + m_3 =$$

$$\overline{A} \cdot \overline{B} \cdot \overline{C} + \overline{A} \cdot \overline{B} \cdot C + \overline{A} \cdot B \cdot \overline{C} + \overline{A} \cdot B \cdot C =$$

