 


Week 3:

Logical Devices

We are here




Decoders



Decoders


 
- Decoders are essentially binary translators.
 - Translate from the output of one circuit to the input of another.
 - Think of them as providing a mapping from a binary number to another encoding.
- Example: one-hot decoder
 - Activates one of four output lines, based on a two-digit binary number. (binary \rightarrow "one-hot")



7-segment decoder





  - Use 7 LEDs to show digits and even letters.




7-segment decoder

  - Common and useful decoder.
 - Translate from a 4-digit binary number to the seven segments of a digital display.
 - Each segment controlled by wire.
 - For each output segment, we'll create Boolean logic for when to turn it on.
 - Example: Segment #0
 - Activate for inputs: 0, 2, 3, 5, 6, 7, 8, 9.
 - In binary: 0000, 0010, 0011, 0101, 0110, 0111, 1000, 1001.





7-segment decoder

 

- Segments are “**active-low**”, meaning they are on when the wire is **low**.
- Example: Displaying digits 0-9
 - Assume input is a 4-digit binary number
 - Segment 0 (top segment) is low whenever the input values are 0000, 0010, 0011, 0101, 0110, 0111, 1000 or 1001, and high whenever input number is 0001 or 0100.
- First step: **Build the truth table and K-map.**

7-segment decoder

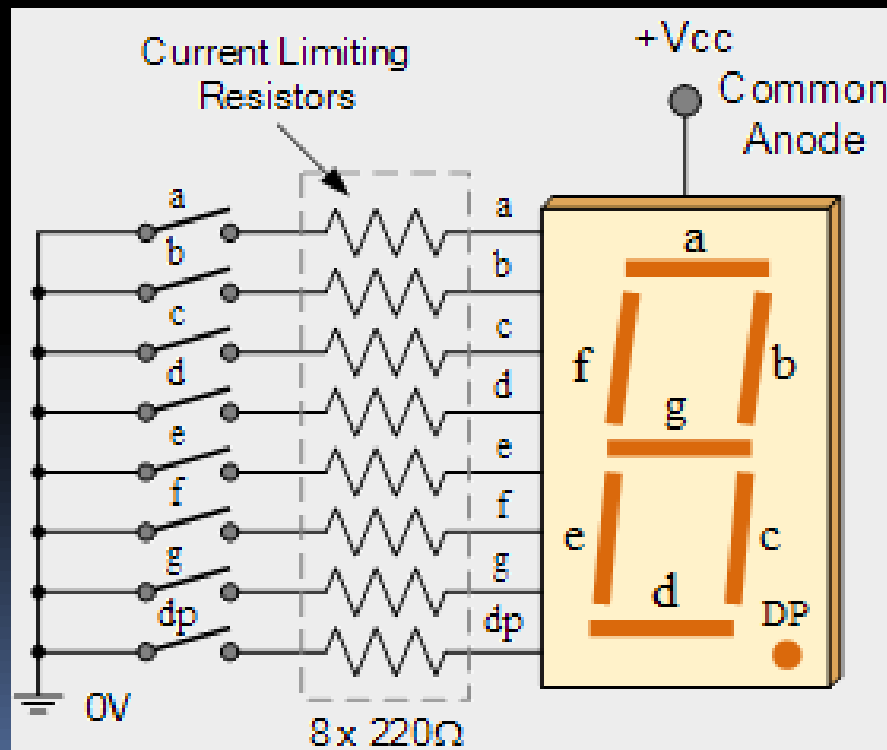 - For 7-seg decoders, turning a segment on involves driving it low.




7-segment decoder

x_3	x_2	x_1	x_0	HEX ₀
0	0	0	0	0
0	0	0	1	1
0	0	1	0	0
0	0	1	1	0
0	1	0	0	1
0	1	0	1	0
0	1	1	0	0
0	1	1	1	0
1	0	0	0	0
1	0	0	1	0

	$\bar{x}_1 \cdot \bar{x}_0$	$\bar{x}_1 \cdot x_0$	$x_1 \cdot x_0$	$x_1 \cdot \bar{x}_0$
$\bar{x}_3 \cdot \bar{x}_2$	0	1	0	0
$\bar{x}_3 \cdot x_2$	1	0	0	0
$x_3 \cdot x_2$?	?	?	?
$x_3 \cdot \bar{x}_2$	0	0	?	?

 - $HEX_0 = \bar{x}_3 \cdot \bar{x}_2 \cdot \bar{x}_1 \cdot x_0 + \bar{x}_3 \cdot x_2 \cdot \bar{x}_1 \cdot \bar{x}_0$
- But what about input values from 1010 to 1111?



“Don’t care” values

- Input values that will never happen or are not meaningful in a given design, and so their output values do not have to be defined.
 - Recorded as 'X' in truth-tables and K-Maps.
- In the K-maps we can think of these “don’t care” values as either 0 or 1 depending on what helps us simplify our circuit.
 - Note you do **NOT** change the X with a 0 or 1, you just include (or not include it) it in a grouping as needed.


“Don’t care” values

- New equation for HEX0:

	$\bar{x}_1 \cdot \bar{x}_0$	$\bar{x}_1 \cdot x_0$	$x_1 \cdot x_0$	$x_1 \cdot \bar{x}_0$
$\bar{x}_3 \cdot \bar{x}_2$	0	1	0	0
$\bar{x}_3 \cdot x_2$	1	0	0	0
$x_3 \cdot x_2$	x	x	x	x
$x_3 \cdot \bar{x}_2$	0	0	x	x

$$\text{HEX0} = \bar{x}_3 \cdot \bar{x}_2 \cdot \bar{x}_1 \cdot x_0 \\ + x_2 \cdot \bar{x}_1 \cdot \bar{x}_0$$

Again for segment 1

 


x_3	x_2	x_1	x_0	HEX ₁
0	0	0	0	0
0	0	0	1	0
0	0	1	0	0
0	0	1	1	0
0	1	0	0	0
0	1	0	1	1
0	1	1	0	1
0	1	1	1	0
1	0	0	0	0
1	0	0	1	0

	$\bar{x}_1 \cdot \bar{x}_0$	$\bar{x}_1 \cdot x_0$	$x_1 \cdot x_0$	$x_1 \cdot \bar{x}_0$
$\bar{x}_3 \cdot \bar{x}_2$	0	0	0	0
$\bar{x}_3 \cdot x_2$	0	1	0	1
$x_3 \cdot x_2$	x	x	x	x
$x_3 \cdot \bar{x}_2$	0	0	x	x

$$\text{HEX1} = x_2 \cdot \bar{x}_1 \cdot x_0 + x_2 \cdot x_1 \cdot \bar{x}_0$$

Again for segment 2

 


x_3	x_2	x_1	x_0	HEX ₂
0	0	0	0	0
0	0	0	1	0
0	0	1	0	1
0	0	1	1	0
0	1	0	0	0
0	1	0	1	0
0	1	1	0	0
0	1	1	1	0
1	0	0	0	0
1	0	0	1	0

	$\bar{x}_1 \cdot \bar{x}_0$	$\bar{x}_1 \cdot x_0$	$x_1 \cdot x_0$	$x_1 \cdot \bar{x}_0$
$\bar{x}_3 \cdot \bar{x}_2$	0	0	0	1
$\bar{x}_3 \cdot x_2$	0	0	0	0
$x_3 \cdot x_2$	x	x	x	x
$x_3 \cdot \bar{x}_2$	0	0	x	x

$$\text{HEX2} = \bar{x}_2 \cdot x_1 \cdot \bar{x}_0$$

The final 7-seg decoder

 - There are many kinds of decoders.
- They all look the same, except for the inputs and outputs.
- Of course, the internals differs from decoder to decoder.
 - ▣ Most devices (e.g., mux) the internals are always the same...



Another “don’t care” example

- Climate control fan:
 - ▣ The fan should turn on ($F=1$) if the temperature is hot ($H=1$) or if the temperature is cold ($C=1$), depending on whether the unit is set to A/C ($A=1$) or heating ($\bar{A}=0$).

H	C	A	F
0	0	0	
0	0	1	
0	1	0	
0	1	1	
1	0	0	
1	0	1	
1	1	0	
1	1	1	

	$\bar{H} \cdot \bar{C}$	$\bar{H} \cdot C$	$H \cdot C$	$H \cdot \bar{C}$
\bar{A}	0	1	X	0
A	0	0	X	1

$$F = A \cdot H + \bar{A} \cdot C$$

Adder circuits



Adders

- Also known as binary adders.
 - Small circuit devices that add two digits together.
 - Combined together to create **iterative combinational circuits**.
- Types of adders:
 - Half adders (HA)
 - Full adders (FA)
 - Ripple Carry Adder
 - Carry-Look-Ahead Adder (CLA)



Review of Binary Math

- Each digit of a decimal number represents a power of 10:

$$258 = 2 \times 10^2 + 5 \times 10^1 + 8 \times 10^0$$

- Each digit of a binary number represents a power of 2:

$$\begin{aligned} 01101_2 &= 0 \times 2^4 + 1 \times 2^3 + 1 \times 2^2 + 0 \times 2^1 + 1 \times 2^0 \\ &= 13_{10} \end{aligned}$$

Unsigned binary addition

- $27 + 53$

$$27 = 00011011$$

$$53 = 00110101$$



1 1 1 1 1 1

00011011

+00110101

01010000



80₁₀

01010000

Unsigned binary addition

▪ $27 + 53$

$27 = 00011011$

$53 = 00110101$



$$\begin{array}{r} 11111 \\ 00011011 \\ + 00110101 \\ \hline \end{array}$$

01010000



80_{10}

01010000

▪ $95 + 181$

01011111

$+10110101$



$$\begin{array}{r} 1111111 \\ 01011111 \\ + 10110101 \\ \hline \end{array}$$

carry out bit



100010100



$20_{10} ??$

00010100

With 8 bits
we can only
represent
unsigned
numbers 0
to 255 !


Half Adders

- A 2-input, 1-bit width binary adder that performs the following computations:

X	0	0	1	1
+Y	+0	+1	+0	+1
<hr/>	<hr/>	<hr/>	<hr/>	<hr/>
CS	00	01	01	10

This is a truth table!

 - A half adder adds two bits to produce a two-bit sum.
- The sum is expressed as a sum bit S and a carry bit C.





Half Adder Implementation

- Equations and circuits for half adder units are easy to define (even without Karnaugh maps)


X	Y	C	S
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0


  
$$C = X \cdot Y \quad S = X \cdot \bar{Y} + \bar{X} \cdot Y \\ = X \oplus Y$$



Full Adders

 

- Similar to half-adders, but with another input Z , which represents a carry-in bit.
 - C and Z are sometimes labeled as C_{out} and C_{in} .
- When Z is 0, the unit behaves exactly like a half adder.
- When Z is 1:

X	0	0	1	1
+Y	+0	+1	+0	+1
+Z	+1	+1	+1	+1
<hr/>	<hr/>	<hr/>	<hr/>	<hr/>
CS	01	10	10	11

Full Adder Design

X	Y	Z	C	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

C	$\overline{Y} \cdot \overline{Z}$	$\overline{Y} \cdot Z$	$Y \cdot Z$	$Y \cdot \overline{Z}$
\overline{X}	0	0	1	0
X	0	1	1	1

S	$\overline{Y} \cdot \overline{Z}$	$\overline{Y} \cdot Z$	$Y \cdot Z$	$Y \cdot \overline{Z}$
\overline{X}	0	1	0	1
X	1	0	1	0

$$C = X \cdot Y + X \cdot Z + Y \cdot Z$$


$$S = X \oplus Y \oplus Z$$

Full Adder Design

- The C term can also be rewritten as:


$$C = X \cdot Y + (X \oplus Y) \cdot Z$$

 - Two terms come from this:
 - ▣ $X \cdot Y = \text{carry generate (G)}$.
 - ▣ $X \oplus Y = \text{carry propagate (P)}$.
- Results in this circuit →




Ripple-Carry Binary Adder

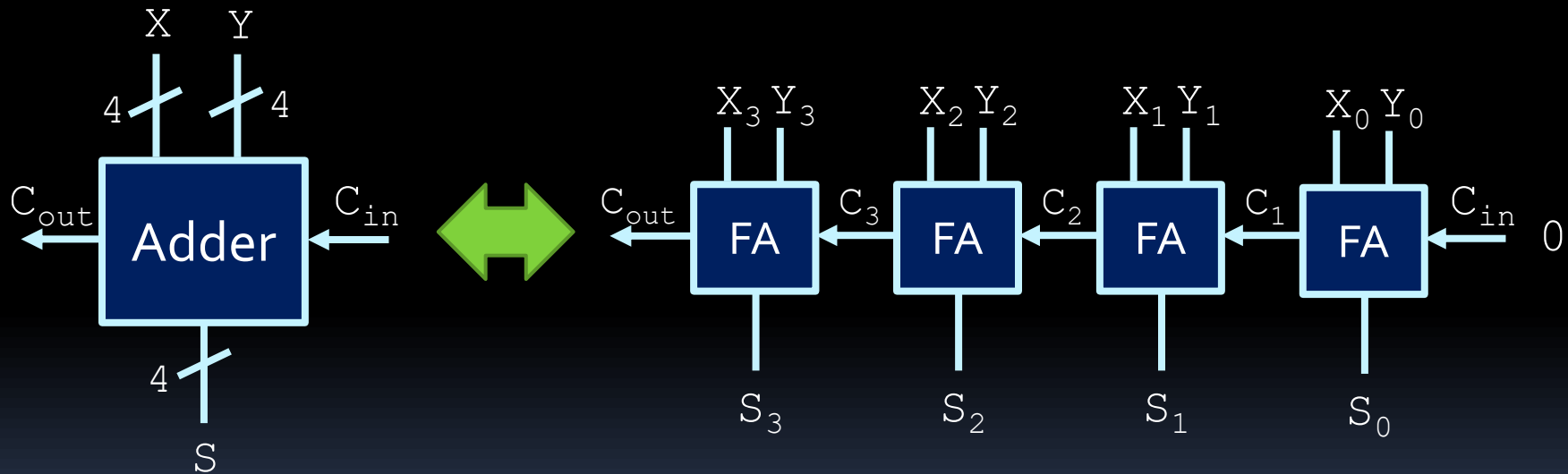- Full adder units are chained together in order to perform operations on signal **vectors**.




The role of C_{in}

 - Why did we use a full-adder for the right-most (smallest) bit? can't we just have a half-adder?
- We could, if we were only interested in addition. But the last bit allows us to do subtraction as well!
 - Time for a little fun with subtraction!



Let's Play a Game!

 1. Choose two **five-digit binary numbers**.
2. Take the **smaller number** and **invert** its digits.
3. Add this inverted number to the larger one.
4. **Add one to the result.**
5. Check what the result is...



Subtractors

- Subtractors are an extension of adders.
 - Basically, perform addition on a negative number.
- To do subtraction, we need to understand **representation** of negative binary numbers.
- **Unsigned numbers**
 - Data bits store the positive version of the number.
- **Sign-and-magnitude:**
 - Use a separate bit for the sign (the sign bit).
- **Signed (2's complement):**
 - Store a negative number using all bits.
 - More common, and **what we use for this course**.

Negative Binary Numbers

- **Unsigned number:**

- All bits are data bits.
- Data bits store a positive number.

- **Example:**

Represent **46** as a 6-bit unsigned number:

bit value	2^5	2^4	2^3	2^2	2^1	2^0
	1	0	1	1	1	0

Negative Binary Numbers

- **Sign and magnitude:**
 - Need to set aside a bit to represent the sign
 - Data bits store the positive version of the number.
- **Example:**

Represent **-18** as a 5-bit plus 1 sign bit:

sign bit	bit value	2^4	2^3	2^2	2^1	2^0
1		1	0	0	1	0

Negative Binary Numbers

- Signed (two's complement)
 - All bits are data bits.
 - Most significant bit (MST) has negative value.
- Example:
Represent **-18** as a 6-bit signed number:

bit value	-2^5	2^4	2^3	2^2	2^1	2^0
	1	0	1	1	1	0

This bit is
worth -32

Convert to Two's Complement

- First get **1's complement**:
 - Invert individual bits (bitwise NOT).
 - Given number X with n bits, this gives $(2^n - 1) - X$

01001101	→	10110010
11111111	→	00000000

- 2's complement = (1's complement + 1)**

01001101	→	10110011
11111111	→	00000001

Know
this!

- Note: Adding a 2's complement number to the original number produces a result of **zero**.

Signed representations

Decimal	Unsigned	Signed 2's
7	111	---
6	110	---
5	101	---
4	100	---
3	011	011
2	010	010
1	001	001
0	000	000
-1	---	111
-2	---	110
-3	---	101
-4	---	100

Practice 2's complement!

- Assume 4-bits signed representation, write the following decimal numbers in binary:

□ 2 => 0010

□ -1 => 1111

□ 0 => 0000

□ 8 => Not possible to represent in 4 digits!

□ -8 => 1000

- What is max positive number?

=> 7 (or $2^{4-1} - 1$)

- What is min negative number?

=> -8 (or -2^{4-1})

Shortcuts for signed numbers

- When thinking of signed binary numbers, there are a few useful tricks to remember:
 - The largest positive binary number is a zero followed by all ones.
 - The binary value for -1 has ones in all the digits.
 - The most negative binary number is a one followed by all zeroes.
- There are 2^n possible values that can be stored in an n -digit binary number.
 - 2^{n-1} are negative, $2^{n-1}-1$ are positive, and one is zero.
 - For example, given an 8-bit binary number:
 - There are 256 possible values
 - One of those values is zero
 - 128 are negative values (11111111 to 10000000)
 - 127 are positive values (00000001 to 01111111)

-1 to -128

1 to 127



Signed subtraction

- Negative numbers are generally stored in 2's complement notation.
 - Reminder: 1's complement \rightarrow bits are the bitwise NOT of the equivalent positive value.
 - 2's complement \rightarrow 1's complement value plus one; results in zero when added to equivalent positive value.
- Subtraction can then be performed by **using the binary adder circuit with negative numbers.**

At the core of subtraction

- Subtraction of a number is simply the addition of its negative value.
- This the negative value is found using the 2's complement process.

- $7 - 3 = 7 + (-3)$

- $-3 - 2 = -3 + (-2)$

Signed Subtraction example

▪ $7 - 3$

$$\begin{array}{r} 0111 \\ -0011 \\ \hline \end{array}$$



$$0111$$

discarded

$$+1101$$



$$\begin{array}{r} 10100 \end{array}$$



$$0100 = 4_{10}$$

▪ $-3 - 2$

$$\begin{array}{r} 1101 \\ -0010 \\ \hline \end{array}$$



$$1101$$

discarded

$$+1110$$



$$\begin{array}{r} 11011 \end{array}$$



$$1011 = -5_{10}$$

What about bigger numbers

▪ $53 - 27$

$$\begin{array}{r} 00110101 \\ -00011011 \\ \hline \end{array}$$



$$00110101$$

discarded

$$+11100101$$



$$\boxed{1}00011010$$



$$00011010 = 26_{10}$$

▪ $27 - 53$

$$\begin{array}{r} 00011011 \\ -00110101 \\ \hline \end{array}$$



$$00011011$$

discarded

$$+11001011$$



$$\boxed{0}11100110$$




$$11100110 = -26_{10}$$

Subtraction circuit


- 4-bit subtractor: $X - Y$
 - X plus 2's complement of Y
 - X plus 1's complement of Y plus 1

Feed 1 as Carry-In in the least significant FA.

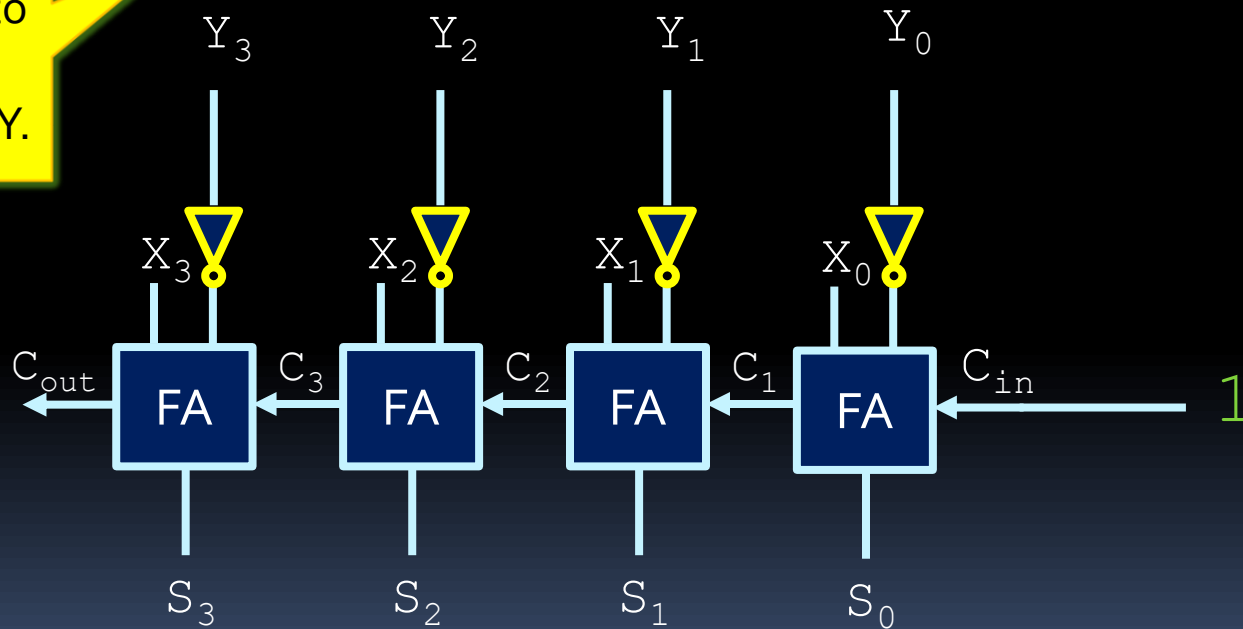Use NOT gates to get the 1's complement of Y .



Addition/Subtraction circuit

 

- The full adder circuit can be expanded to incorporate the subtraction operation
 - Remember: 2's complement = 1's complement + 1
 - We connect Sub to Cin

Food for Thought

- What happens if we add these two positive signed binary numbers $0110 + 0011$ (i.e., $6 + 3$)?
 - The result is 1001 .
 - But that is a negative number (-7)! ☹️
- What happens if we add the two negative numbers $1000 + 1111$ (i.e., $-8 + (-1)$)?
 - The result is 0111 with a carry-out. ☹️
- We need to know when the result might be wrong.
 - This is usually indicated in hardware by the **Overflow** flag!
 - More about this when we'll talk about processors.