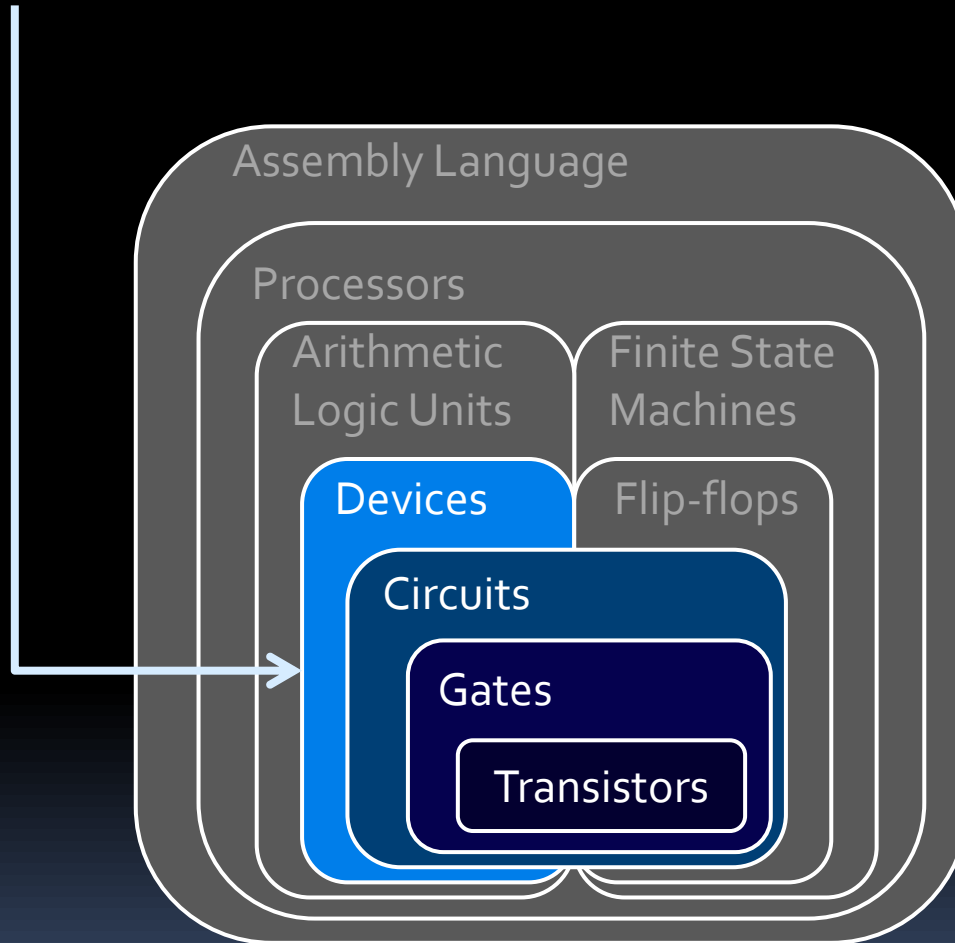


Week 4: Sequential Circuits

Last Week



Build A Counter?


- Can you build a device that counts number of key presses?
 - After key is pressed once, hex display should show 1
 - After key is pressed again, show 2
 - Third time: show 3
 - Then reset to 0

Something else to consider..

- Computer specs use terms like “16 GB of RAM” and “5GHz processors”.
 - What do these terms mean?
 - **RAM** = Random Access Memory
 - 16GB = 16 billion chars (bytes)
 - 5 **GHz** = 5 billion clock pulses per second.
 - But what does this mean in circuitry?
 - How do you use circuits to store values?
 - What is the purpose of a clock signal?



This Week

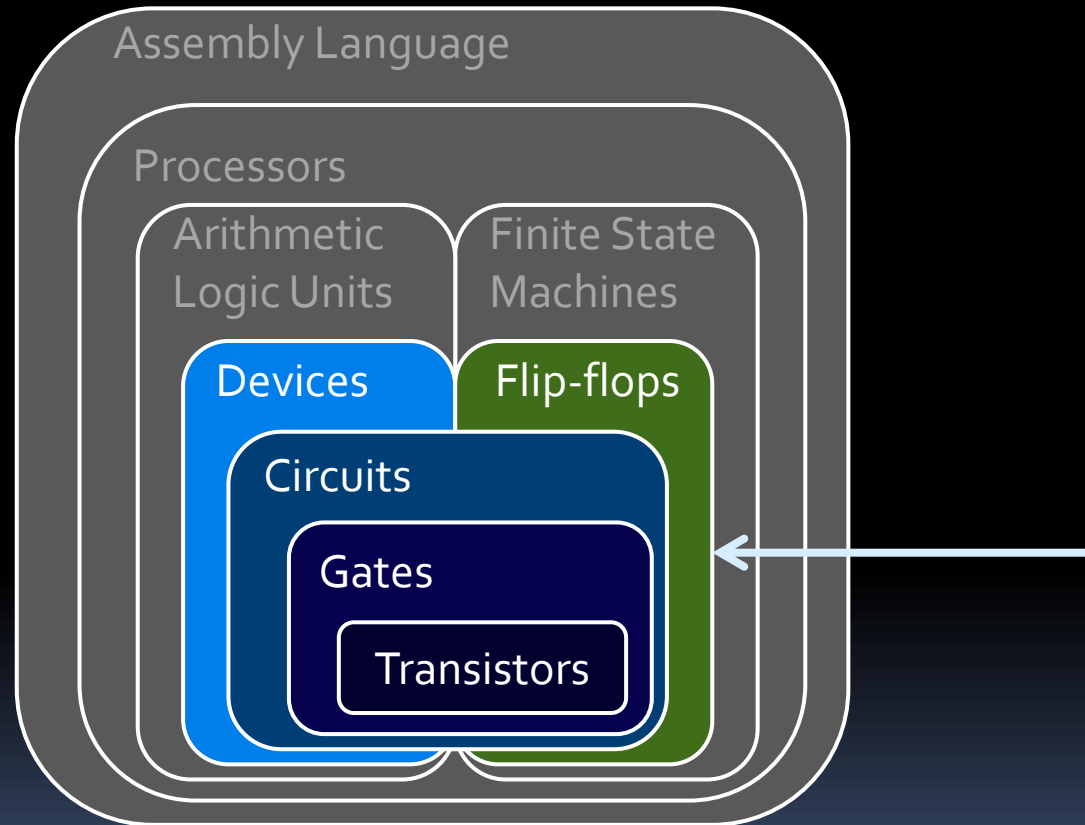


Two kinds of circuits

- So far, we've dealt with **combinational circuits**:
 - Circuits where the output values are entirely dependent and predictable from the input values.
- Another class of circuits: **sequential circuits**
 - Circuits that also depend on both the inputs **and the previous state** of the circuit.



Sequential circuits

 - This creates circuits whose internal state can change over time, where the same input values can result in different outputs.
- Why would we need circuits like this?
 - Memory values
 - Reacting to changing inputs




Creating sequential circuits

  - Essentially, sequential circuits have feedback in the circuit.
 - How is this accomplished?
 - What is the result of having the output of a component or circuit be connected to its input?



Storing and Reusing Values

 - I want to store the output of an AND gate and reuse it as input.





- Does the following work?



- How do we **reason** about this circuit?

Waveform Diagrams

  


Propagation Delay

- Outputs don't change instantaneously.
 - Electrons have to move, transistors open/close...
 - Even in combinatorial circuits!
- **Gate Delay** or **Propagation Delay**:
 - “The length of time it takes for an input change to result in the corresponding output change.”


Max propagation delay

 - This is the longest possible delay for a circuit.
- Slowest path from any input to any output.
 - In terms of **total propagation delay**, not path length or number of components on it.




Max propagation delay

 
- This is the longest possible delay for a circuit.
- Slowest path from any input to any output.
 - In terms of **total propagation delay**, not path length or number of components on it.




Gate Delays

 

Ideal

 


Considering delays

 

Feedback Circuit Example (AND)

- Let's analyze it

 


Q_T and Q_{T+1}
represent the values
of Q at a time T , and
a point in time
immediately after
($T+1$)

A	Q_T	Q_{T+1}
0	0	0
0	1	0
1	0	0
1	1	1

Feedback Circuit Example (AND)

- Let's analyze it

 

Q_T and Q_{T+1} represent the values of Q at a time T , and a point in time immediately after ($T+1$)


A	Q_T	Q_{T+1}
0	0	0
0	1	0
1	0	0
1	1	1

If $A=0$, Q_{T+1} becomes 0 no matter what Q_T was.

What happens next for later values of A ?

Feedback Circuit Example (AND)

- Let's analyze it

 

Q_T and Q_{T+1} represent the values of Q at a time T, and a point in time immediately after ($T+1$)

A	Q_T	Q_{T+1}
0	0	0
0	1	0
1	0	0
1	1	1

If $A=0$, Q_{T+1} becomes 0 no matter what Q_T was.


What happens next for later values of A?

Q_{T+1} gets stuck at 0 and cannot change ☹️

AND with feedback


- Some gates don't have useful results when outputs are fed back into inputs.
- Once Q becomes 0, it stays stuck as 0.

A	Q_T	Q_{T+1}
0	0	0
0	1	0
1	0	0
1	1	1

 

OR with feedback

 - Some gates don't have useful results when outputs are fed back into inputs.



In this truth table, Q_T and Q_{T+1} represent the values of Q at a time T , and a point in time immediately after ($T+1$)

A	Q_T	Q_{T+1}
0	0	0
0	1	1
1	0	1
1	1	1



If $A=1$, Q_{T+1} becomes 1 no matter what Q_T was.

What happens next for later values of A ?

Q_{T+1} gets stuck at 1. Not very useful ☹

Feedback Examples (NAND, NOR)

  
- NAND, NOR gates w/ feedback have more interesting characteristics, which lend themselves to storage devices.



- What makes NAND and NOR feedback circuits different?
 - Unlike the AND and OR gate circuits (which get stuck), the output Q_{T+1} can be changed, based on A .

Feedback Example (NAND)

 
- Let's assume we set $A=0$
 - Then, output Q will go to 1.
 - If we leave A unchanged we can store 1 indefinitely!



A	Q_T	Q_{T+1}
0	0	1
0	1	1
1	0	1
1	1	0

Feedback Example (NAND)

 - Let's assume we set $A=0$
 - Then, output Q will go to 1.
 - If we leave A unchanged we can store 1 indefinitely!
- If we set $A=1$, Q 's value can change, but there's a catch!




What happens in these last two scenarios?


A	Q_T	Q_{T+1}
0	0	1
0	1	1
1	0	1
1	1	0

Unsteady state!
Can't store 0 long!

NAND waveform behaviour

 

A	Q_T	Q_{T+1}
0	0	1
0	1	1
1	0	1
1	1	0

 


Gate delay. Output does not change instantaneously

This is known as **oscillation**.
The circuit oscillates between high and low.

Feedback Example (NOR)

 - Let's assume we set $A=1$
- Then, output Q will go to 0.
- If we leave A unchanged we can store 0 indefinitely!
- If we flip A , we can change Q , but there's a catch here too!



A	Q_T	Q_{T+1}
0	0	1
0	1	0
1	0	0
1	1	0

Feedback behaviour

- NAND behaviour


A	Q_T	Q_{T+1}
0	0	1
0	1	1
1	0	1
1	1	0

- NOR behaviour

A	Q_T	Q_{T+1}
0	0	1
0	1	0
1	0	0
1	1	0

- Output Q_{T+1} can be changed, based on A.
- However, gates like these that feed back on themselves enter an **unstable state**.
 - The output is not stable – it **oscillates**.

NAND waveform behaviour

 

A	Q_T	Q_{T+1}
0	0	1
0	1	1
1	0	1
1	1	0



We want to avoid this. We should be able to store high and low values for as long as we want, and change those values as needed.

Unstable Storage


- We almost have storage.
 - But we can't have this unstable feedback.
- Need to be able to set high or reset to low whenever we want, and maintain these.

The Quest for Storage

- We need a feedback circuit with stable behaviour:
 - We should be able to set to 0 or to 1
 - Circuit should maintain state for long-term.
 - No instability.

Latches


 
- Combine multiple NAND or NOR gates to get stable behaviour.




- These circuits are called **latches**.

- The $\bar{S}\bar{R}$ Latch

  - ...or $S'R'$ or $\sim S \sim R$ and so on



Quick Reminder


 


Knowing $A = 0$, what can you say about the output of this NAND gate?

- Output must be 1, regardless of the other input
- i.e., a zero input **"locks"** the NAND gate



$\overline{S}\overline{R}$ latch: case 1

  - Let's see what happens when the input values are changed...
 - Assume that \overline{S} and \overline{R} are set to 1 and 0 to start.
 - The \overline{R} input sets the output \overline{Q} to 1, which sets the output Q to 0.
 - Setting \overline{R} to 1 keeps the output value \overline{Q} at 1, which maintains both output values.




$\overline{S}\overline{R}$ latch: case 2

  - (continuing from previous)
 - ▣ \overline{S} and \overline{R} start with values of 1, when \overline{S} is set to 0.
 - ▣ This sets output Q to 1, which sets the output \overline{Q} to 0.
 - ▣ Setting \overline{S} back to 1 keeps the output value \overline{Q} at 0, which maintains both output values.




Conclusion

- The input 11 maintains the previous output state!
- Same input, different outputs.
- It's the **sequence** of inputs that matters.

 


Case 1

 

Case 2


$\overline{S}\overline{R}$ latch

 

\overline{S}	\overline{R}	Q_T	\overline{Q}_T	Q_{T+1}	\overline{Q}_{T+1}
0	0	X	X	1	1
0	1	X	X	1	0
1	0	X	X	0	1
1	1	0	1	0	1
1	1	1	0	1	0

- \overline{S} and \overline{R} are called “set” and “reset” respectively.
- Note how the circuit “remembers” its signal when going from 10 or 01 to 11.
- Going from 00 to 11 produces a **race condition**:
 - We don’t know what the output will be. It can be 0 or 1, depending on which input changes first. This causes unstable behaviour.

SR latch


 


S	R	Q_T	\bar{Q}_T	Q_{T+1}	\bar{Q}_{T+1}
0	0	0	1	0	1
0	0	1	0	1	0
0	1	X	X	0	1
1	0	X	X	1	0
1	1	X	X	0	0

- In this case, S and R are “set” and “reset”.
- In this case, the circuit “remembers” previous output when going from 10 or 01 to 00.
- As with $\bar{S}\bar{R}$ latch, unstable behaviour is possible, but this time when inputs go from 11 to 00.

SR latch timing diagram

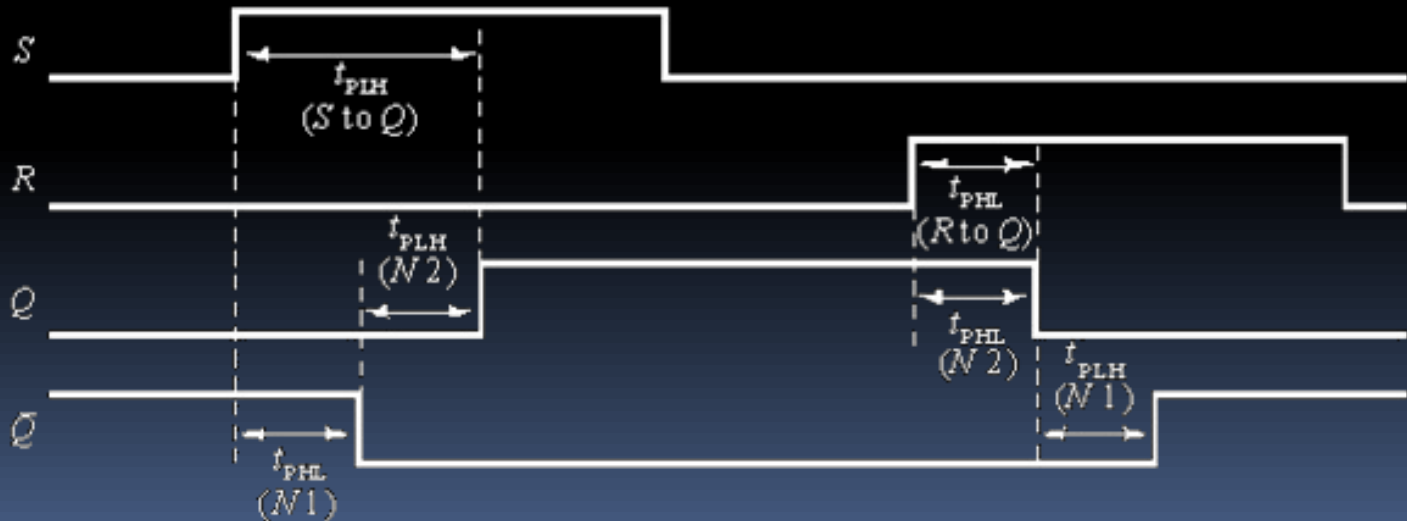 - Important to note that the output signals don't change instantaneously.



Summary: S'R' and SR latches

$\bar{S}\bar{R}$ -latch

\bar{S}	\bar{R}	Q_T	\bar{Q}_T	Q_{T+1}	\bar{Q}_{T+1}	
0	0	X	X	1	1	Forbidden state
0	1	X	X	1	0	Set Q to 1
1	0	X	X	0	1	Reset Q to 0
1	1	0	1	0	1	Maintain Q
1	1	1	0	1	0	

"set" and "reset"
cannot be both true!

SR-latch

S	R	Q_T	\bar{Q}_T	Q_{T+1}	\bar{Q}_{T+1}	
0	0	0	1	0	1	Maintain Q
0	0	1	0	1	0	
0	1	X	X	0	1	Reset Q to 0
1	0	X	X	1	0	Set Q to 1
1	1	X	X	0	0	Forbidden state

Reading from latches


- We now have circuits that can store values.
- But how do we distinguish:
 - “5 highs in a row” vs “10 highs in a row”
 - “001100” vs “010”
- Impose some frequency for reading the signal?
 - But when can we sample (read) the signal?
- Need some sort of timing signal, to let the circuit know when the output may be sampled.
 - clock signals.

Why A Clock




- How do we distinguish between:
 - “high 5 times in a row”
 - “high 10 times in a row”
- What do “5 times” or “10 times” mean?
- Need a way to tell when a signal (input or output) is “ready” to be sampled

Clock Signals

 

 - **Clock**: a regular signal, where high value indicates that the output of the latch may be sampled.
- Usually drawn as:



- But looks more like:



Clock Frequency

- **Frequency** = the number of pulses occur per second.
 - measured in Hertz (Hz).
- Higher frequency → can do more every second.

5 Hz



1 second

19 Hz




1 second

Signal Restrictions

- What limits the clock frequency?

 - Circuit complexity
 - Max propagation delay!
- Physical limits
 - Latency of transistors
- Manufacturing variations
- Physical clock limits
 - Gibbs phenomenon
 - Jitter




Beyond the scope
of CSCB58

Signal Restrictions

- CPU makers try to increase it every year.
- 40 years ago: 1 Mhz
 - Apple II – MOS 6502
 - C64 – MOS 6510
- Today: 3-5 GHz
- x 5000 increase in 40 years!


Clocked SR latch

 

- Adding another layer of NAND gates to the $\bar{S}\bar{R}$ latch gives us a **clocked SR latch** (or **gated SR latch**)
- Basically, a latch with a control input signal C.
- The input C is often connected to a clock signal


Clocked SR latch behaviour

 - Same behaviour as SR latch, but with timing:
 - Start off with $S=0$ and $R=1$, like earlier example.
 - If clock is high, the first NAND gates invert those values, which get inverted again in the output.
 - Setting both inputs to 0 maintains the output values.




Clocked SR latch behaviour

 - Continued from previous:
 - Now set the clock low.
 - Even if the inputs change, the low clock input prevents the change from reaching the second stage of NAND gates.
 - Result: the clock needs to be high in order for the inputs to have any effect.




Clocked SR latch - summary

 

The S and R signals are only allowed to affect the circuit when the clock input (C) is high.


- When clock is high, behave like a SR latch.
- When clock is low, S and R are blocked and there is no way to change the output.

Clocked SR latch

 

- This is the typical symbol for a clocked SR latch.
- Note: the small NOT circle after the Q output is simply the notation to use to denote the inverted output value. It's not an extra NOT gate.


Clocked SR latch behaviour

 

Q_T	S	R	Q_{T+1}	Result
0	0	0	0	no change
0	0	1	0	reset
0	1	0	1	set
0	1	1	?	???
1	0	0	1	no change
1	0	1	0	reset
1	1	0	1	set
1	1	1	?	???

- Wait!
- Where's the clock?
- There's a better way to look at this....

Clocked SR latch behaviour

 

C	S	R	Q_{T+1}	Result
0	X	X	Q_T	no change
1	0	0	Q_T	no change
1	0	1	0	reset
1	1	0	1	set
1	1	1	?	Undefined

- Assuming the clock is 1, we still have a problem when S and R are both 1, since the state of Q is indeterminate.
- **A better design** would prevent S and R from both going high at the same time.