

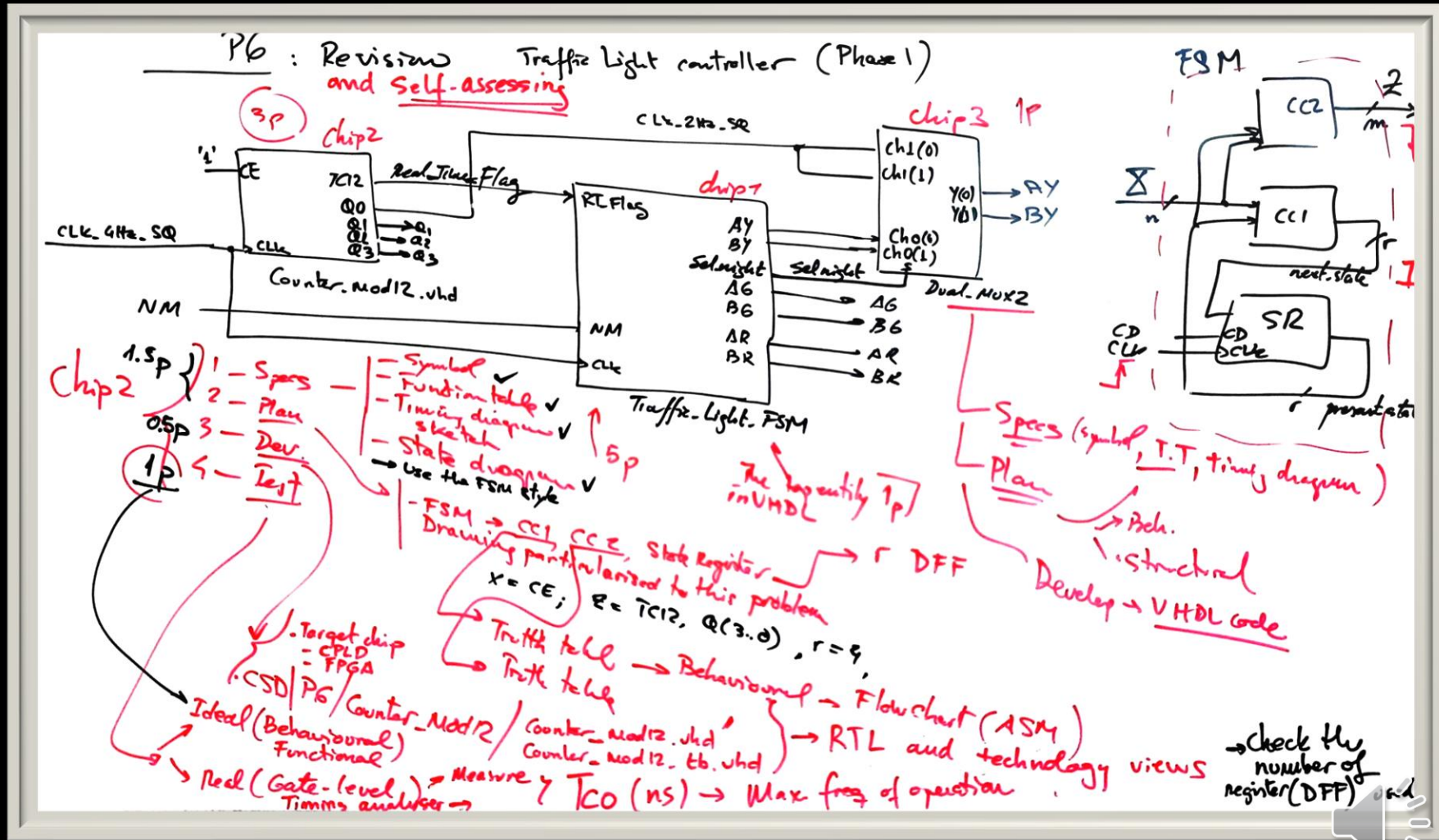


Week 5, part D: FSM Design

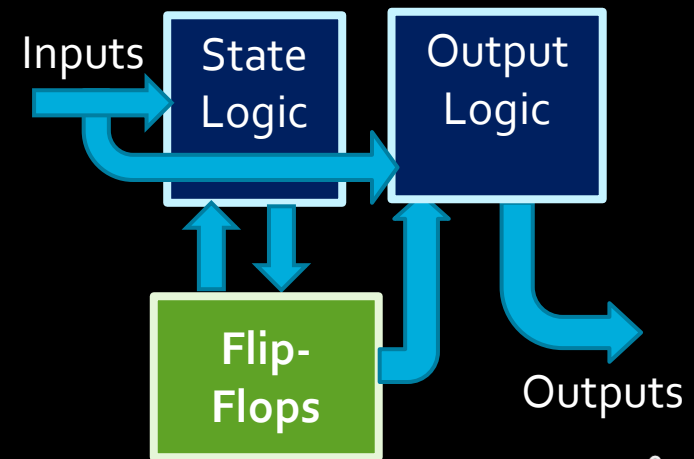



FSM Design Steps

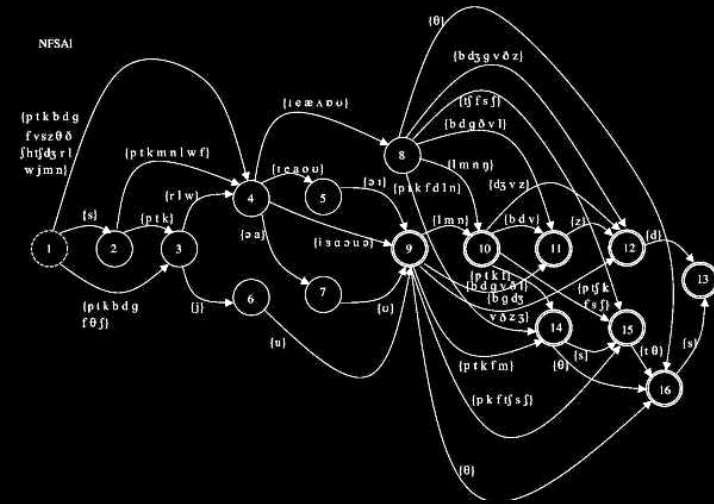1. Draw **state diagram**
2. Derive **state table** from state diagram
3. Assign **flip-flop value configuration** to each state
 - At least $\lceil \log_2(\# \text{ of states}) \rceil$ flip-flops
4. **Redraw** state table with flip-flop values
5. Derive **combinational circuit** for output and for each flip-flop input
 - State logic: figure out next state
 - Output logic: figure out output



State Diagrams with output

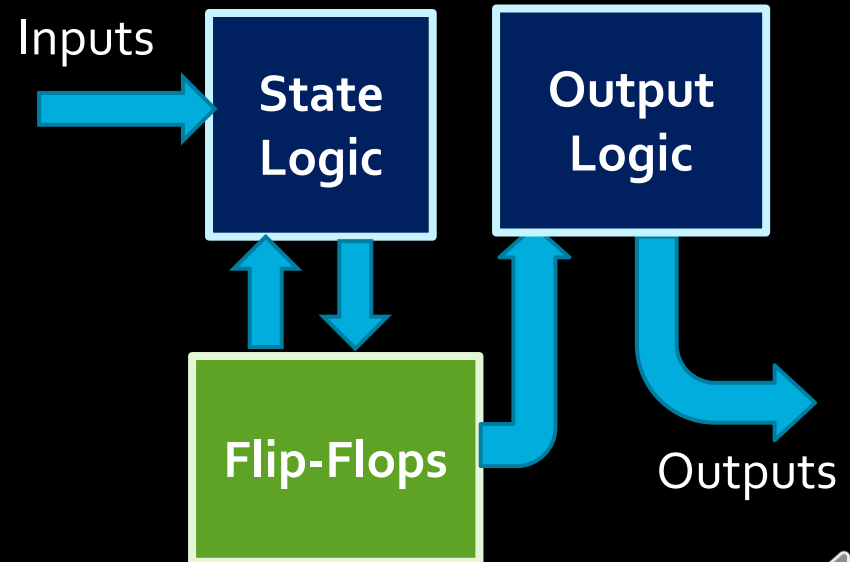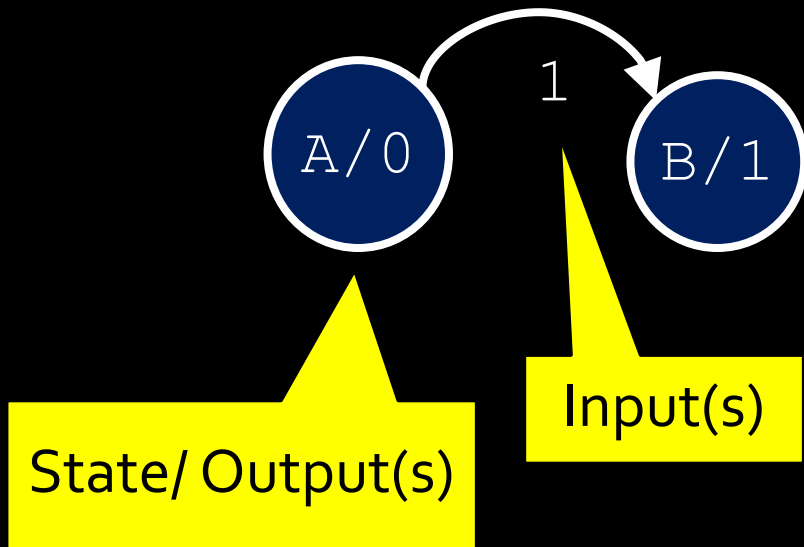- For now, let's assume output only depends on current state.




Example #4: Sequence Recognizer

- Recognize a sequence of input values, and raise a signal if that input has been seen.
- Example: **Three high values in a row**
 - Detect that the input has been high for three rising clock edges.
 - Assumes a single input IN and a single output Z .
- **What are the states?**



Step 1: State diagram

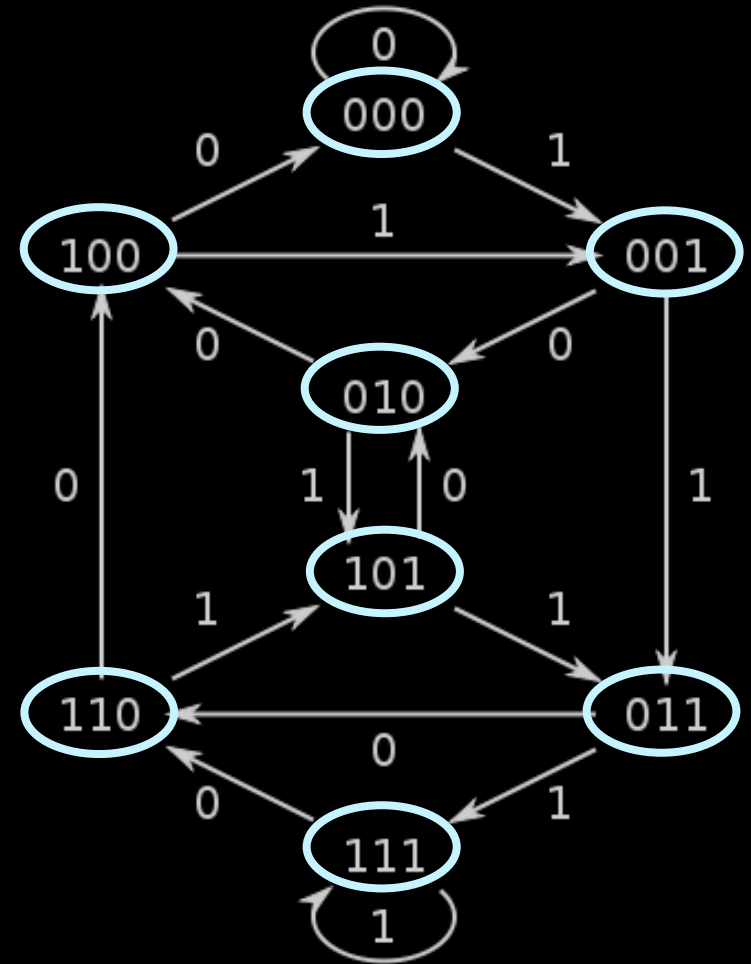- In this case, we will label states with the **three most recent input bits**.
- Transitions between states depends on the input IN.
- Indicated by the values on the transition arrows.



Step 2: State table

- Make sure that the state table lists **all the states** in the state diagram, and **all the possible inputs** that can occur at that state.

Previous State	Input	Next State
"000"	0	"000"
"000"	1	"001"
"001"	0	"010"
"001"	1	"011"
"010"	0	"100"
"010"	1	"101"
"011"	0	"110"
"011"	1	"111"
"100"	0	"000"
"100"	1	"001"
"101"	0	"010"
"101"	1	"011"
"110"	0	"100"
"110"	1	"101"
"111"	0	"110"
"111"	1	"111"




Step 3: Assign flip-flops

- The flip-flops are responsible for storing state.
- A single flip-flop can store either 0 or 1
→ supports two states.
- How many states can be stored with each additional flip-flop?
 - One flip-flop → 2 states
 - Two flip-flops → 4 states
 - Three flip-flops → 8 states
 - ...
 - Eight flip-flops? → $2^8 = 256$ states

For n states we need
 $\lceil \log_2(n) \rceil$ flip-flops



How many flip-flops for this one?

 


3



Step 3: Assign flip-flops

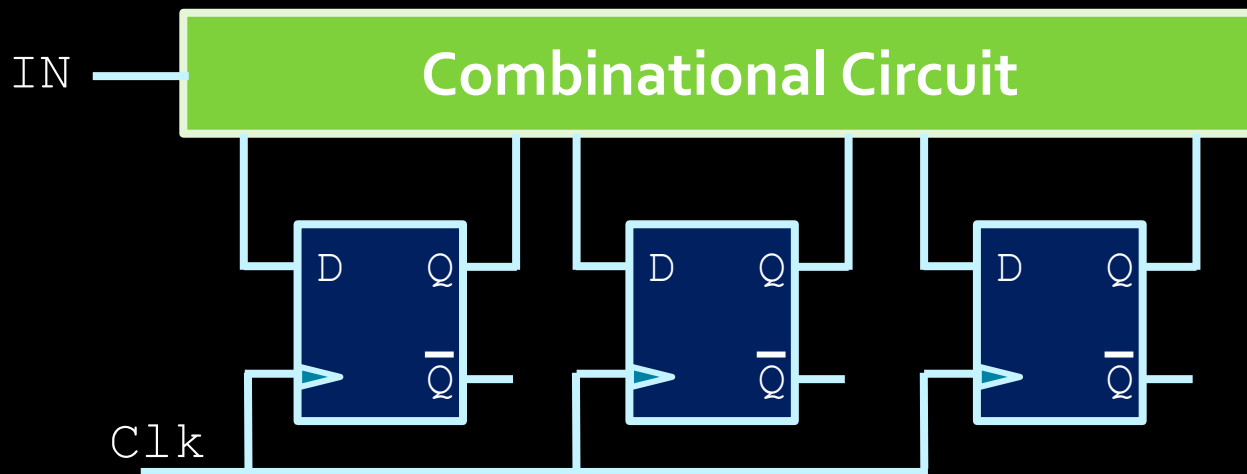- In this case, we need to store 8 states.
 - ▣ 8 states = 3 flip-flops ($3 = \log_2 8$)
- For now, assign a flip-flop to each digit of the state names in the FSM & state table.



Step 4: State table

- Usually, the states have names that don't map over to flip-flops so easily.

Prev. State	IN	Next State
"000"	0	"000"
"000"	1	"001"
"001"	0	"010"
"001"	1	"011"
"010"	0	"100"
"010"	1	"101"
"011"	0	"110"
"011"	1	"111"
"100"	0	"000"
"100"	1	"001"
"101"	0	"010"
"101"	1	"011"
"110"	0	"100"
"110"	1	"101"
"111"	0	"110"
"111"	1	"111"



Step 4: State table

- Usually, the states have names that don't map over to flip-flops so easily.
- It may be an easy mapping, but is it a good one?
 - ▣ Not really, but we'll get to why later.

prev state (input)				next state (output)		
F ₂	F ₁	F ₀	IN	F ₂	F ₁	F ₀
0	0	0	0	0	0	0
0	0	0	1	0	0	1
0	0	1	0	0	1	0
0	0	1	1	0	1	1
0	1	0	0	1	0	0
0	1	0	1	1	0	1
0	1	1	0	1	1	0
0	1	1	1	1	1	1
1	0	0	0	0	0	0
1	0	0	1	0	0	1
1	0	1	0	0	1	0
1	0	1	1	0	1	1
1	1	0	0	1	0	0
1	1	0	1	1	0	1
1	1	1	0	1	1	0
1	1	1	1	1	1	1



Step 5: Circuit design

- Karnaugh map for $F_{2(\text{next})}$:

	$\overline{F_0} \cdot \overline{IN}$	$\overline{F_0} \cdot IN$	$F_0 \cdot IN$	$F_0 \cdot \overline{IN}$
$\overline{F_2} \cdot \overline{F_1}$	0	0	0	0
$\overline{F_2} \cdot F_1$	1	1	1	1
$F_2 \cdot F_1$	1	1	1	1
$F_2 \cdot \overline{F_1}$	0	0	0	0

$$F_{2(\text{next})} = F_1$$

Next state

Current state



Step 5: Circuit design

- Karnaugh map for $F_{1(\text{next})}$:

	$\overline{F_0} \cdot \overline{IN}$	$\overline{F_0} \cdot IN$	$F_0 \cdot IN$	$F_0 \cdot \overline{IN}$
$\overline{F_2} \cdot \overline{F_1}$	0	0	1	1
$\overline{F_2} \cdot F_1$	0	0	1	1
$F_2 \cdot F_1$	0	0	1	1
$F_2 \cdot \overline{F_1}$	0	0	1	1

$$F_{1(\text{next})} = F_0$$



Step 5: Circuit design

- Karnaugh map for $F_{0(next)}$:


	$\overline{F_0} \cdot \overline{IN}$	$\overline{F_0} \cdot IN$	$F_0 \cdot IN$	$F_0 \cdot \overline{IN}$
$\overline{F_2} \cdot \overline{F_1}$	0	1	1	0
$\overline{F_2} \cdot F_1$	0	1	1	0
$F_2 \cdot F_1$	0	1	1	0
$F_2 \cdot \overline{F_1}$	0	1	1	0

$$F_{0(next)} = IN$$



Step 5: Circuit design

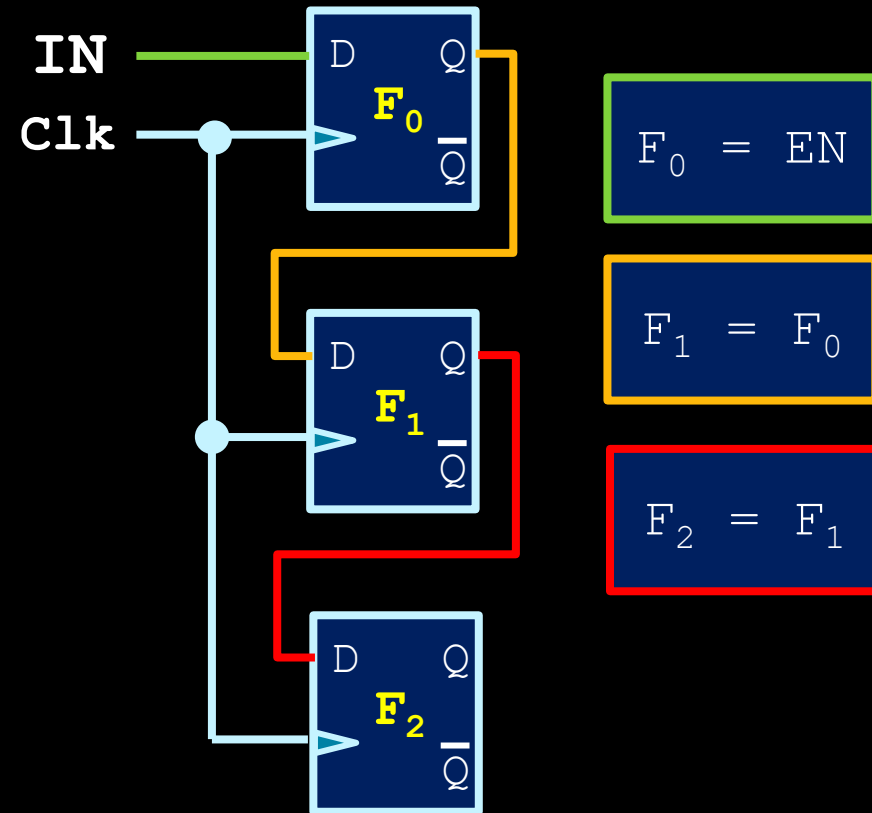
- Resulting circuit looks like the circuit on the right →
- Will record the state and make the state transitions happen based on the input
- It makes sense: we want to look at the last 3 bits.
 - $F_2 = \text{old } F_1$
 - $F_1 = \text{old } F_0$
 - $F_0 = \text{IN}$



Step 5: Circuit design

- What about the output Z?
 - Z should go high when we see **three high in a row**.
 - When state is **111**
- Boolean equation for Z:

$$Z = F_0 \cdot F_1 \cdot F_2$$

 



Defining outputs

- Two ways to design the output of a state machine:
 - **Moore machine:**
 - The output for the FSM depends solely on the **current state**.
 - **Mealy machine:**
 - FSM output depends on **both the state and the input** (based on input actions).
 - Being in state X can result in different output, depending on the input that caused that state.





Moore Machines

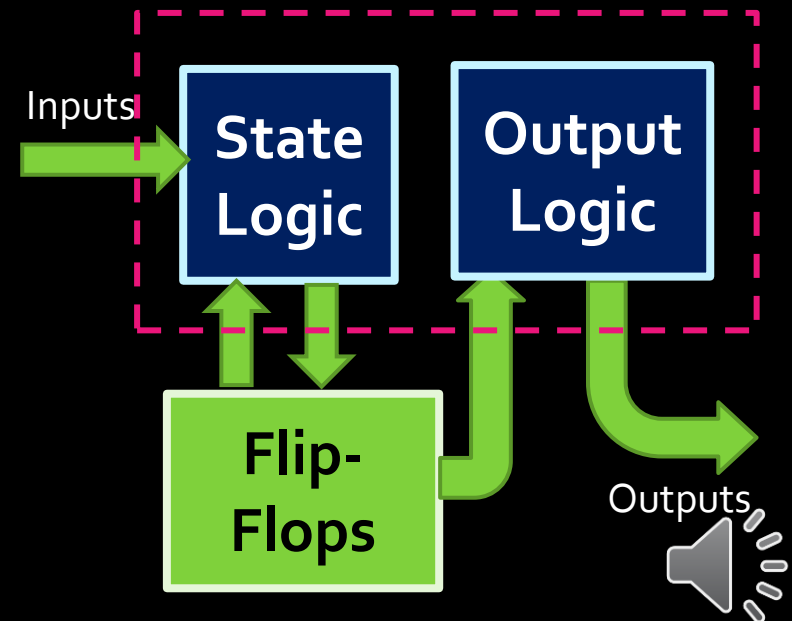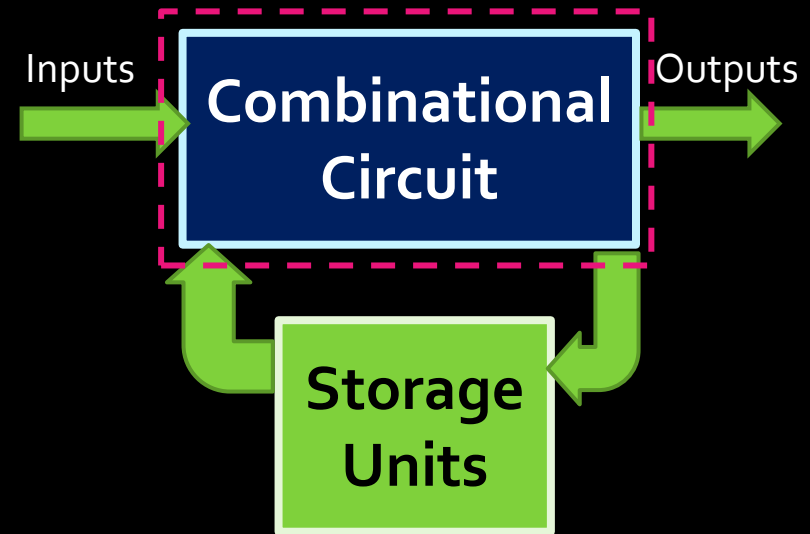- Output is determined solely based on current state
 - Flip-flop values.
- For simplicity, most of our examples will focus on Moore machines.



Mealy Machines

 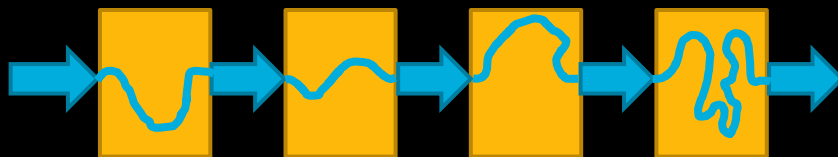
- Output is determined by both the **current state** and the **current input values**.
- Long paths of connected Mealy machines **may** be combinatorial!




State diagrams with output

- Output values are incorporated into the state diagram, depending on the type of machine.

➤ Moore Machine

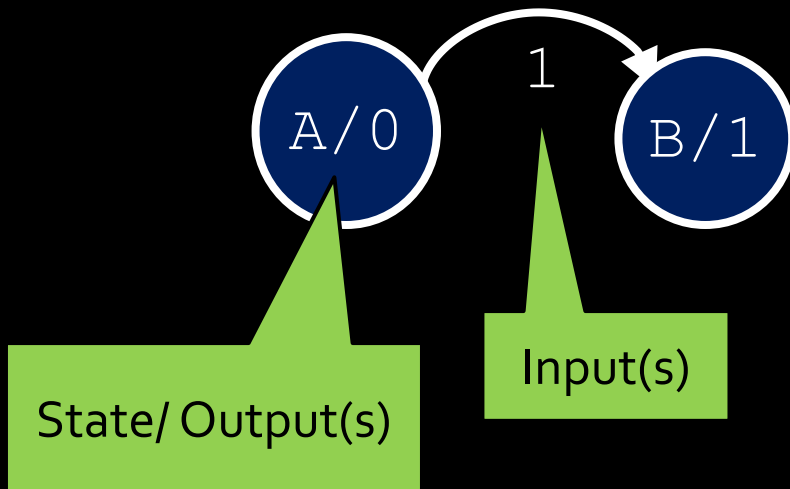

➤ Mealy Machine

 



Moore vs Mealy

Moore

Pros:

- A bit simpler.
- Always a flip-flop between input and output
 - No long combinatorial paths:

Cons:

- May need more states and flip-flops.
- Takes at least one cycle to respond to input

Mealy

Cons:

- Potentially long path from input to output does not go through a flip-flop.
 - Output is transparent

Pros:


- Sometimes need fewer states / FFs for same task
- Output can respond sooner to inputs.



FSM design


■ Design steps for FSM:

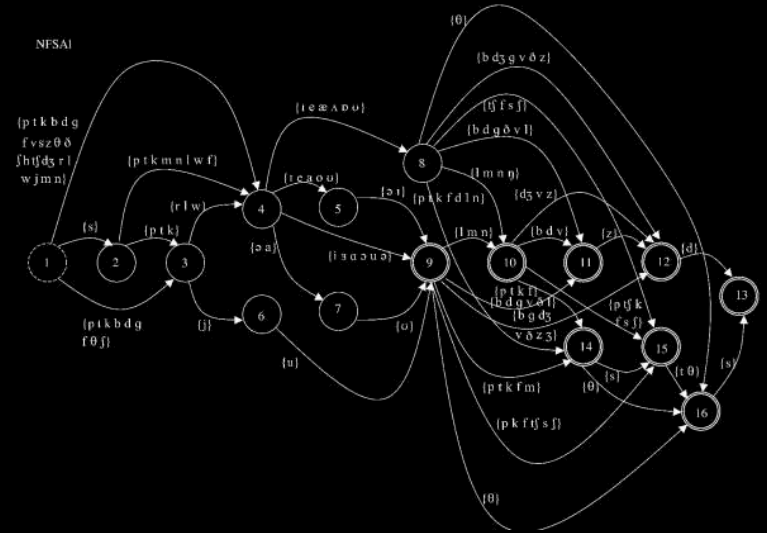1. Draw **state diagram**
2. Derive **state table** from state diagram
3. Assign **flip-flop configuration** to each state
4. Redraw state table as **truth table** using flip-flop values
5. Derive **combinational circuit** for output and for each flip-flop.



Timing and Unsafe Transitions

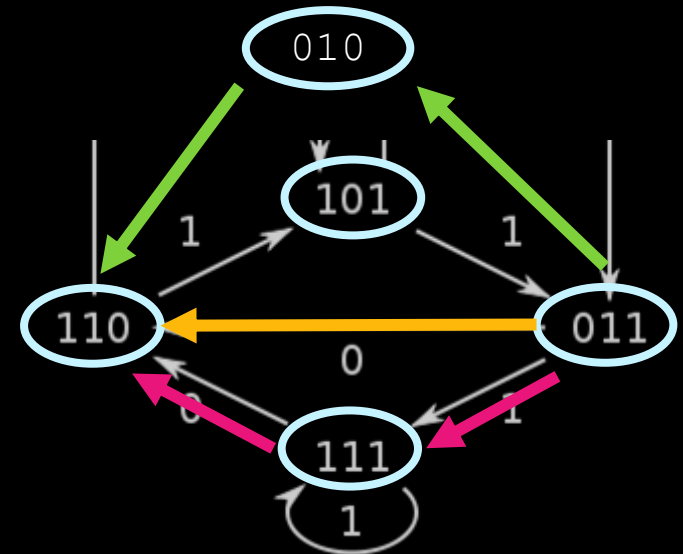
- Example: if recognizer circuit is in state **011** and gets the input **0**, it moves to state **110**.
- The first and last flipflops should change “**at the same time**”, but they can’t.
- This **race condition** can be unsafe.
 - If the **first flip-flop changes first**, the state will change to **111**, and **the output would go high for an instant**, which is unexpected behaviour.
 - If the **second flip-flop changes first**, it is fine since the intermediate state **010** has the same low output.



Timing and state assignments

- So how do you solve this?
- Possible solutions:
 1. Whenever possible, make flip-flop assignments such that neighbouring states differ by at most one flip-flop value (**state encoding differs by one bit**).
 2. If “intermediate” state output is the **same as starting or destination state** → no problem
 3. **Add intermediate transition states** between start and end
 - (Use unused flip-flop states or may need to **add more**)



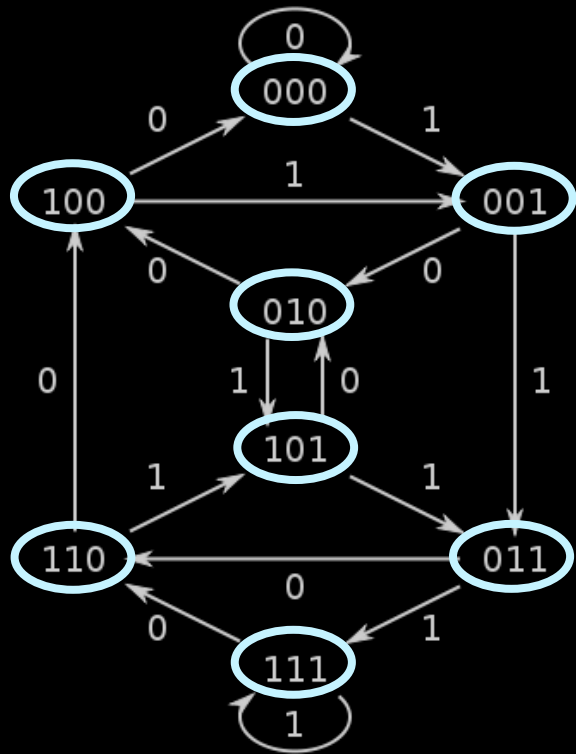

Previous State	IN	Next State
000	0	000
000	1	001
001	0	010
001	1	011
010	0	100
010	1	101
011	0	110
011	1	111
100	0	000
100	1	001
101	0	010
101	1	011
110	0	100
110	1	101
111	0	110
111	1	111

State **000** does not have to have flip-flop values **000**, it can be anything you want to assign.

Try to re-assign the states so the timing issue doesn't exist



Food for thought?

Try to think about the following at home:

1. Can you re-assign the flip-flop configuration to avoid the dangerous transition?
2. How many states do you need to recognize an n -bit pattern?
3. Can we do better?
 - Come to the review on Tuesday!



Question #4

- How would we make the following Finite State Machine?



<https://youtu.be/Vi4LmILZUog>




Example #5


- Exploding Pen
 - Starts disarmed
 - 3 clicks to arm
 - 3 clicks to disarm
- Is this a good design?
- How do we build it?
 - Note: Please do not use the knowledge you've gained in this course to develop exploding pens.
 - Note 2: If you do, please don't use them for evil




Step 1: State Diagram

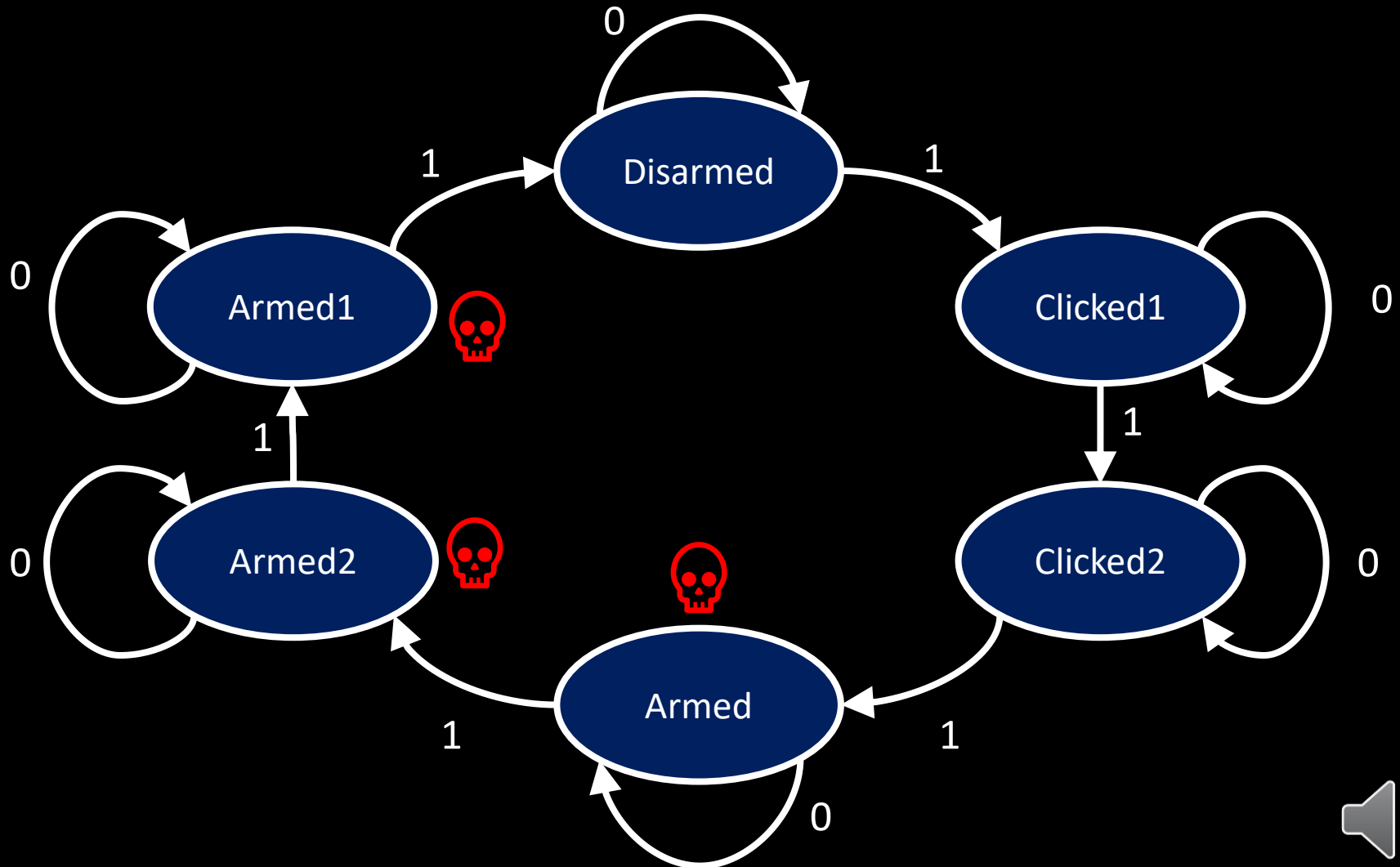

Step 1: State Diagram

 


Step 2: State Table

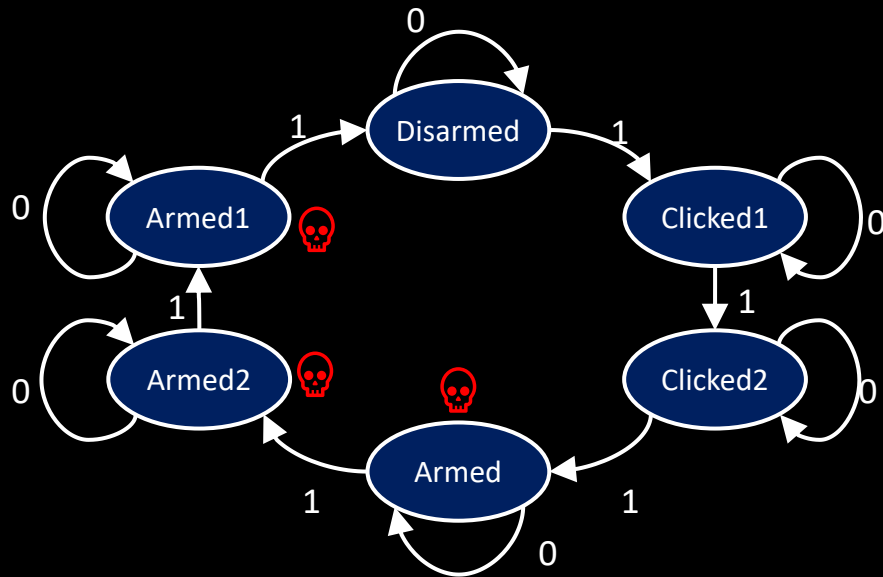

Previous State	Input	Next State




Step 2: State Table

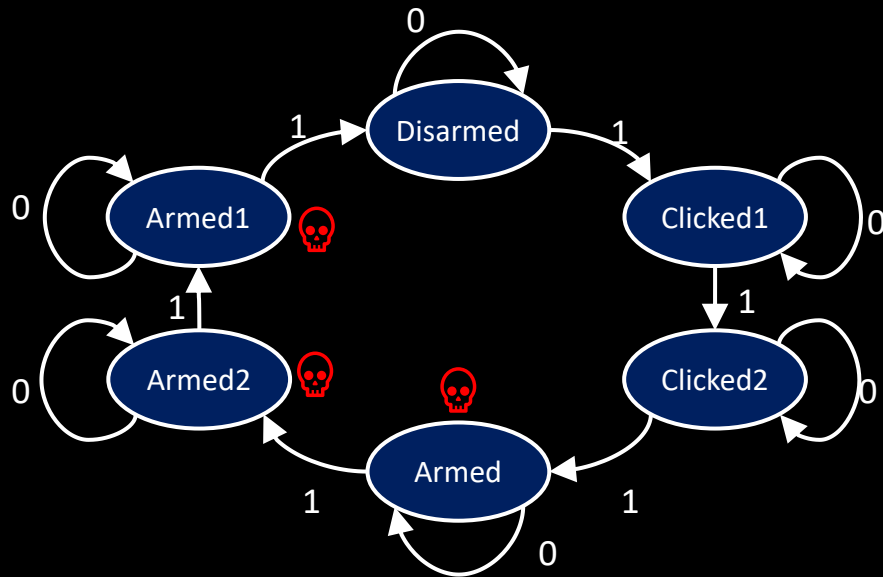

Previous State	Input	Next State
Disarmed	0	
Disarmed	1	




Step 2: State Table

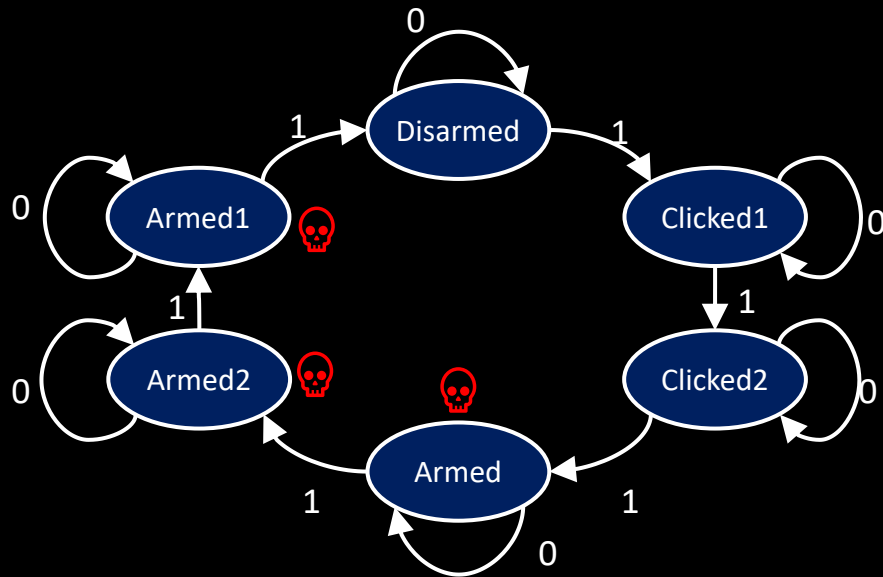

Previous State	Input	Next State
Disarmed	0	
Disarmed	1	
Clicked1	0	
Clicked1	1	
Clicked2	0	
Clicked2	1	
Armed	0	
Armed	1	
Armed2	0	
Armed2	1	
Armed1	0	
Armed1	1	



Step 2: State Table

 

Previous State	Input	Next State
Disarmed	0	Disarmed
Disarmed	1	Clicked1
Clicked1	0	Clicked1
Clicked1	1	Clicked2
Clicked2	0	Clicked2
Clicked2	1	Armed
Armed	0	Armed
Armed	1	Armed2
Armed2	0	Armed2
Armed2	1	Armed1
Armed1	0	Armed1
Armed1	1	Disarmed



Step 3: FlipFlop Assignment

- Let's just try the standard binary order.


State	F_2	F_1	F_0
Disarmed	0	0	0
Clicked1	0	0	1
Clicked2	0	1	0
Armed	0	1	1
Armed2	1	0	0
Armed1	1	0	1



Step 3: FlipFlop Assignment

- Not safe!
- Transition from Clicked₁ to Clicked₂ might go through **Armed**!

State	F ₂	F ₁	F ₀
Disarmed	0	0	0
Clicked1	0	0	1
Clicked2	0	1	0
Armed	0	1	1
Armed2	1	0	0
Armed1	1	0	1

 

Step 3: FlipFlop Assignment

- Much nicer: **one bit change for all transitions.**
- Also: F_2 is high if and only if state is armed!

State	F_2	F_1	F_0
Disarmed	0	0	0
Clicked1	0	0	1
Clicked2	0	1	1
Armed	1	1	1
Armed2	1	1	0
Armed1	1	0	0




Step 4: Update State Table

F_2	F_1	F_0	Input	F_2	F_1	F_0
0	0	0	0	0	0	0
0	0	0	1	0	0	1
0	0	1	0	0	0	1
0	0	1	1	0	1	1
0	1	1	0	0	1	1
0	1	1	1	1	1	1
1	1	1	0	1	1	1
1	1	1	1	1	1	0
1	1	0	0	1	1	0
1	1	0	1	1	0	0
1	0	0	0	1	0	0
1	0	0	1	0	0	0



Step 5: Circuit Design

 

F_0	$\overline{F_0}\overline{C}$	$\overline{F_0}C$	F_0C	$F_0\overline{C}$
$\overline{F_2}\overline{F_1}$	0	1	1	1
$\overline{F_2}F_1$	X	X	1	1
F_2F_1	0	0	0	1
$F_2\overline{F_1}$	0	0	X	X

F_1	$\overline{F_0}\overline{C}$	$\overline{F_0}C$	F_0C	$F_0\overline{C}$
$\overline{F_2}\overline{F_1}$	0	0	1	0
$\overline{F_2}F_1$	X	X	1	1
F_2F_1	1	0	1	1
$F_2\overline{F_1}$	0	0	X	X

F_2	$\overline{F_0}\overline{C}$	$\overline{F_0}C$	F_0C	$F_0\overline{C}$
$\overline{F_2}\overline{F_1}$	0	0	0	0
$\overline{F_2}F_1$	X	X	1	0
F_2F_1	1	1	1	1
$F_2\overline{F_1}$	1	0	X	X



Circuit Design

State Logic

$$F_2 = F_2 \overline{\text{Click}} + F_1 \text{Click}$$

$$F_1 = F_1 \overline{\text{Click}} + F_0 \text{Click}$$

$$F_0 = F_0 \overline{\text{Click}} + \overline{F_2} \text{Click}$$

Output Logic

$$Y = F_2$$



Circuit Design

Wait a
minute!

State Logic

$$F_2 = \overline{F_2 \text{Click}} + F_1 \text{Click}$$

$$F_1 = \overline{F_1 \text{Click}} + F_0 \text{Click}$$

$$F_0 = \overline{F_0 \text{Click}} + \overline{F_2} \text{Click}$$

Output Logic

$$Y = F_2$$



Circuit Design

These
are
muxes!



State Logic

$$F_2 = \overline{F_2 \text{Click}} + F_1 \text{Click}$$


$$F_1 = \overline{F_1 \text{Click}} + F_0 \text{Click}$$

$$F_0 = \overline{F_0 \text{Click}} + \overline{F_2} \text{Click}$$


Output Logic

$$Y = F_2$$

Click

 

Circuit

 

We've gone quite far!

- We know how to build combinatorial and synchronous circuits.
- Starting next time, **we will learn to build computers**

