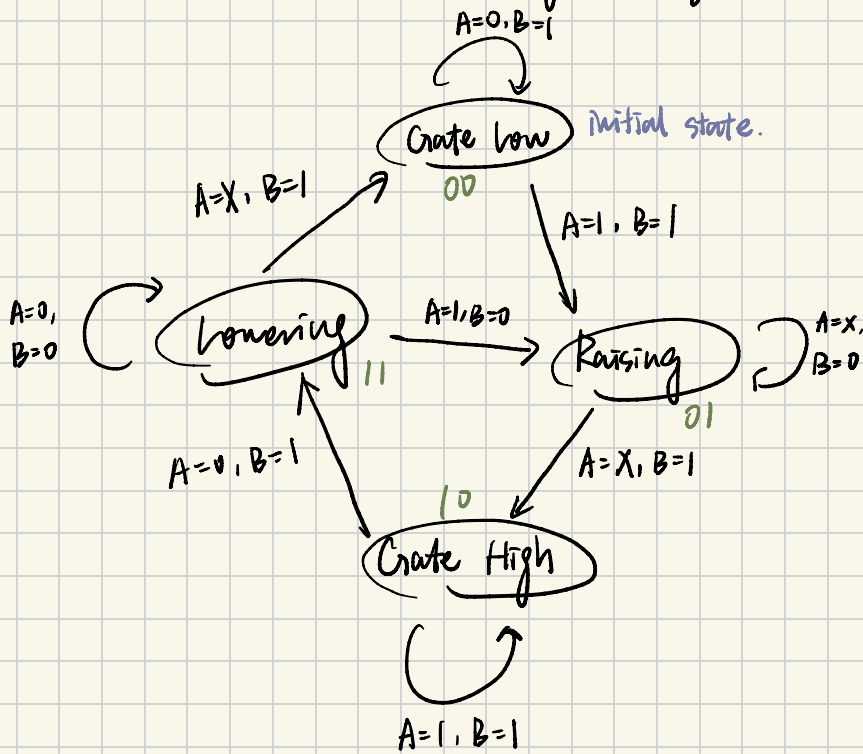


Jreying Group 1009388066

Part: A

Input: A, B

Transition: Gate low, Raising, Gate High, Lowering.



Current State	Input A	Input B	Next State
Gate low 00	0	1	Gate low 00
Gate low 00	1	1	Raising 01
Raising 01	X	0	Raising 01
Raising 01	X	1	Gate High 10
Gate High 10	1	1	Gate High 10
Gate High 10	0	1	Lowering 11
Lowering 11	0	0	Lowering 11
Lowering 11	1	0	Raising 01
Lowering 11	X	1	Gate low 00

3. 4 states \Rightarrow we need ^{minimum} $\log_2(4) = 2$ flip-flops for state machine.

4. Gate Low = 00
 Raising = 01
 Gate High = 10
 Lowering = 11

5. Truth Table.

F_1	F_0	Input A	Input B	new F_1	new F_0
0	0	0	1	0	0
0	0	1	1	0	1
0	1	X	0	0	1
0	1	X	1	1	0
1	0	1	1	1	0
1	0	0	1	1	1
1	1	0	0	1	1
1	1	1	0	0	1
1	1	X	1	0	0

K-map.

new \bar{F}_1

	$\bar{A} \cdot \bar{B}$	$\bar{A} \cdot B$	$A \cdot B$	$A \cdot \bar{B}$
$\bar{F}_1 \cdot \bar{F}_0$	X	0	0	X
$\bar{F}_1 \cdot F_0$	0	1	1	0
$F_1 \cdot F_0$	1	0	0	0
$F_1 \cdot \bar{F}_0$	X	1	1	X

$$\text{new } \bar{F}_1 = F_1 \cdot \bar{F}_0 + \bar{A} \cdot \bar{B} \cdot F_1 + B \cdot \bar{F}_1 \cdot F_0$$

new \bar{F}_2

	$\bar{A} \cdot \bar{B}$	$\bar{A} \cdot B$	$A \cdot B$	$A \cdot \bar{B}$
$\bar{F}_1 \cdot \bar{F}_0$	X	0	1	X
$\bar{F}_1 \cdot F_0$	1	0	0	1
$F_1 \cdot F_0$	1	0	0	1
$F_1 \cdot \bar{F}_0$	X	1	0	X

$$\text{new } \bar{F}_2 = \bar{A} \cdot \bar{B} + A \cdot \bar{B} + \bar{A} \cdot F_1 \cdot \bar{F}_0 + A \cdot \bar{F}_1 \cdot \bar{F}_0$$

Part II: Output.

1. Moore Machine

2. Output

	$F_1 F_0$	Output R	Output L
Gate low	00	0	0
Raising	01	1	0
Gate high	10	0	0
Lowering	11	0	1

$$R = \overline{F_1} \cdot F_0$$

$$L = F_1 \cdot F_0$$