 


Week 5 Review


Max propagation delay

- This is the longest possible delay for a circuit.
- Slowest path from any input to any output.
 - In terms of **total propagation delay**, not path length or number of components on it.




Practice Question 1

 - Build a 16-to-1 mux from 4-to-1 muxes that have a maximum propagation delay of 5 nanoseconds
- It must finish within one clock cycle.
- What is the minimum safest clock cycle for our circuit?
- → 10ns




Practice Question 2

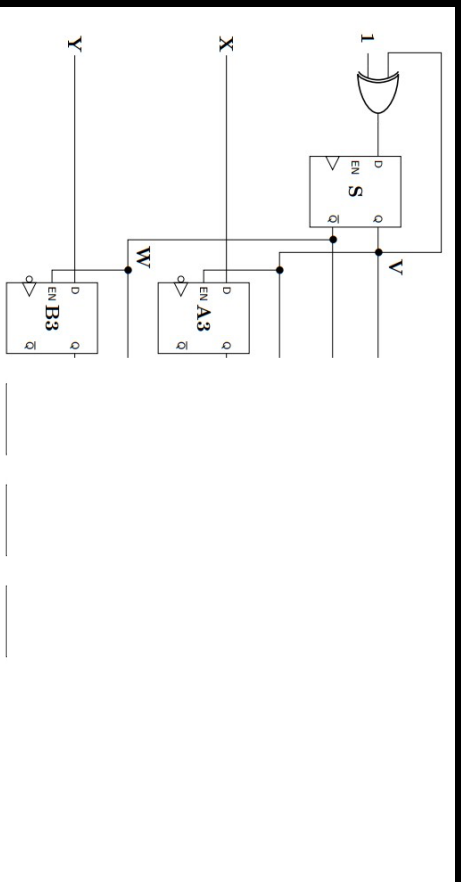

- The flip-flop S is triggered on the _____ edge of the clock, while the flip-flops A3, B3 are triggered on the _____ edge of the clock

Practice Question 2


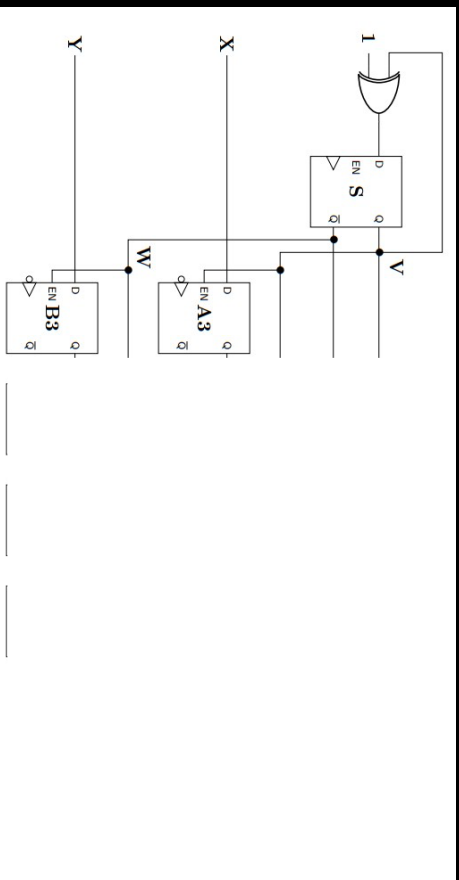


- The flip-flop S is triggered on the rising edge of the clock, while the flip-flops A3, B3 are triggered on the falling edge of the clock

Practice Question 3

Draw
V and W
given CLK.

Assume S is
zero at the
beginning.

 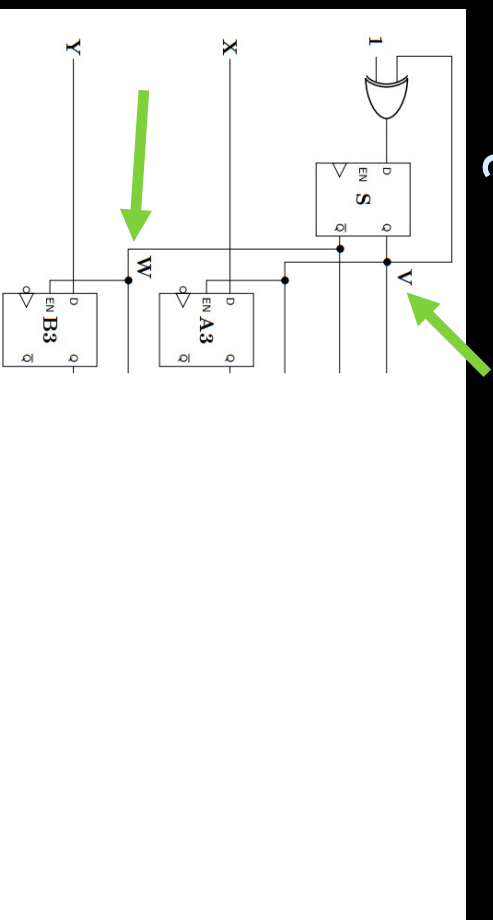



Practice Question 3

Draw
V and W

given CLK.

Assume S is
zero at the
beginning.

Hint: what is this?

  



Practice Question 3

Draw
V and W

given CLK.

Assume S is
zero at the
beginning.

Hint: what is this?
this is a T-Flipflop

  



Practice Question 3

Draw

V and W



given CLK.

Assume S is
zero at the
beginning.

  



Practice Question 4

  - Assuming the Q output of both flip-flops starts as low ($X=0$ $Y=0$).
- What will the values of X and Y be over the next few clock cycles?
- (These are positive edge-triggered)





Practice Question 4

  - Assuming the Q output of both flip-flops starts as low ($X=0$ $Y=0$).
- What will the values of X and Y be over the next few clock cycles?
 - (These are positive edge-triggered)





Practice Question 4

  - Given the circuit on the right and the input waveform below, what will the outputs be on Q_L and Q_F ?
 - Initial state for both is zero




Practice Question 4

- Given the circuit on the right and the input waveform below, what will the outputs be on Q_L and Q_F ?
- Initial state for both is zero

  

Question 5


- You have this counter:

 

- How do you make a signal Y that goes high after exactly 10 clock cycles?

Question 5

- You have this counter:

 


- How do you make a signal Y that goes high after exactly 10 clock cycles?

$$Y = Q_3 \underline{Q_2} Q_1 \underline{Q_0}$$

Question 6


- You have this counter:

 

- How do you make a signal Y that goes high **every** 10 clock cycles?

Question 6


- You have this counter:

 

- How do you make a signal Y that goes high **every 10 clock cycles**?
 - $Y = Q_3 \overline{Q_2} Q_1 \overline{Q_0}$ ← is this good enough?

Question 6


- You have this counter:

 

- How do you make a signal Y that goes high **every 10 clock cycles**?
 - $Y = Q_3 \overline{Q_2} Q_1 \overline{Q_0}$ ← is this good enough?
 - No! This Y goes high every 16 cycles!

Question 6

- You have this counter:

 

- How do you make a signal Y that goes high **every** 10 clock cycles?
 - $Y = Q_3 \overline{Q_2} Q_1 \overline{Q_0}$
 - $\text{Clear} = Y \leftarrow$ set to zero after reaching 10!